




Si CMOS for RF Power Applications

J. A. del Alamo
MIT


Workshop on Advanced Technologies for Next Generation of RFIC
2005 RFIC Symposium
June 12, 2005

Sponsors: DARPA, IBM, SRC

RF power applications

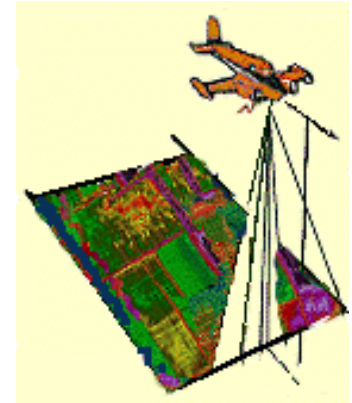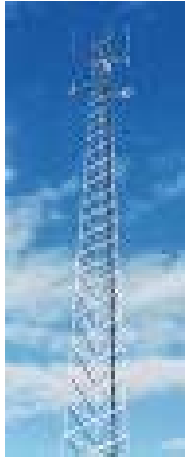
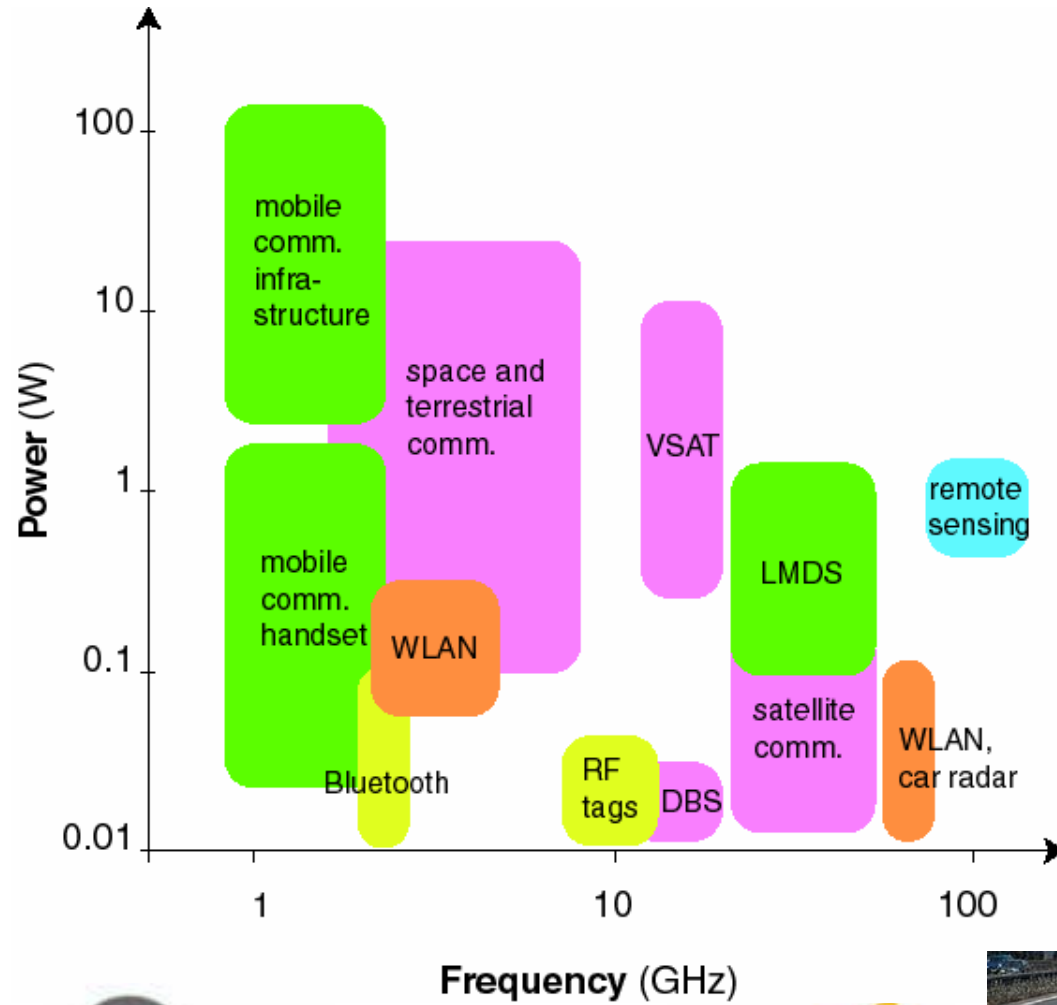


Power vs. frequency

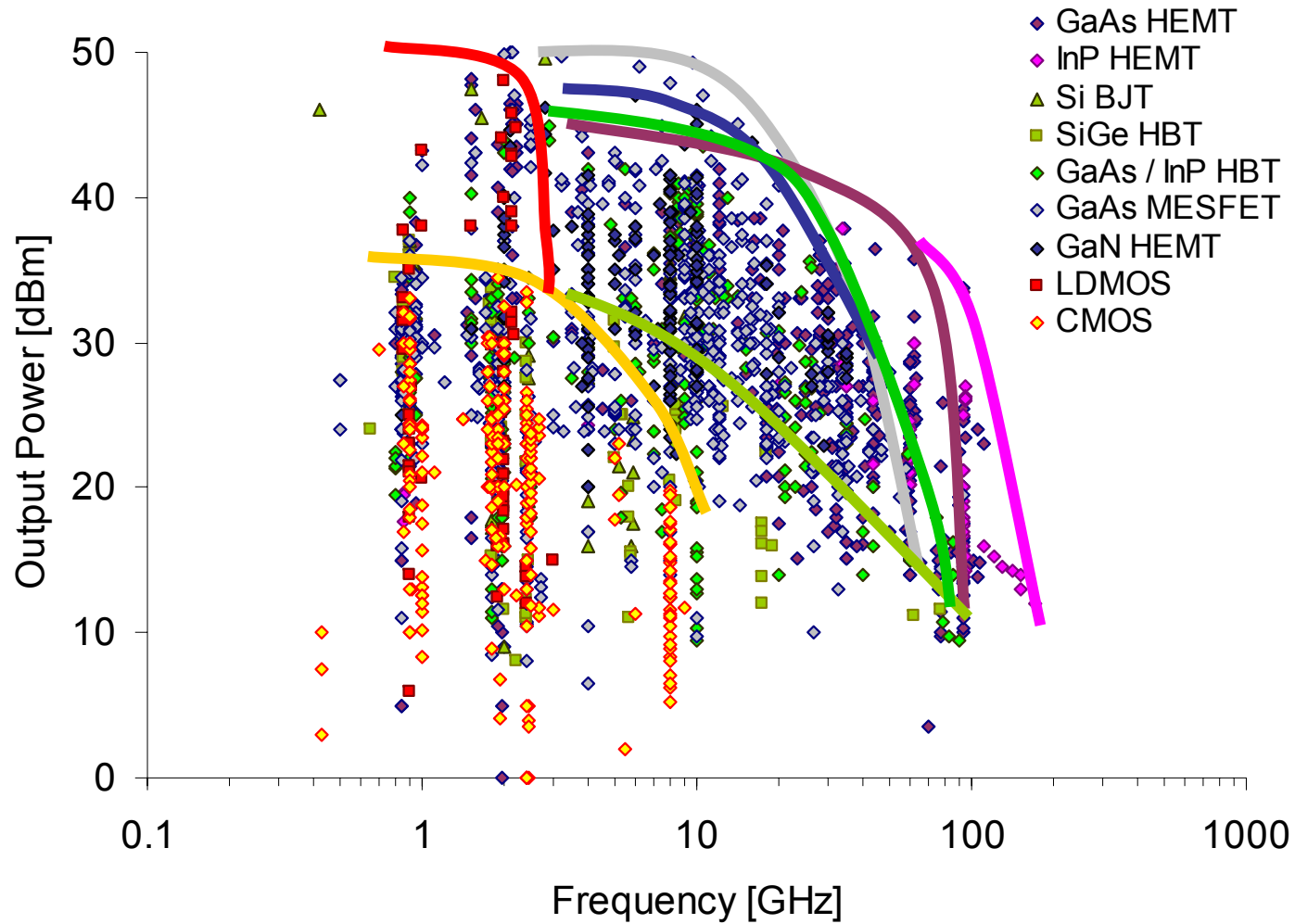


Compilation of research papers from IEEE Xplore by J. Scholvin

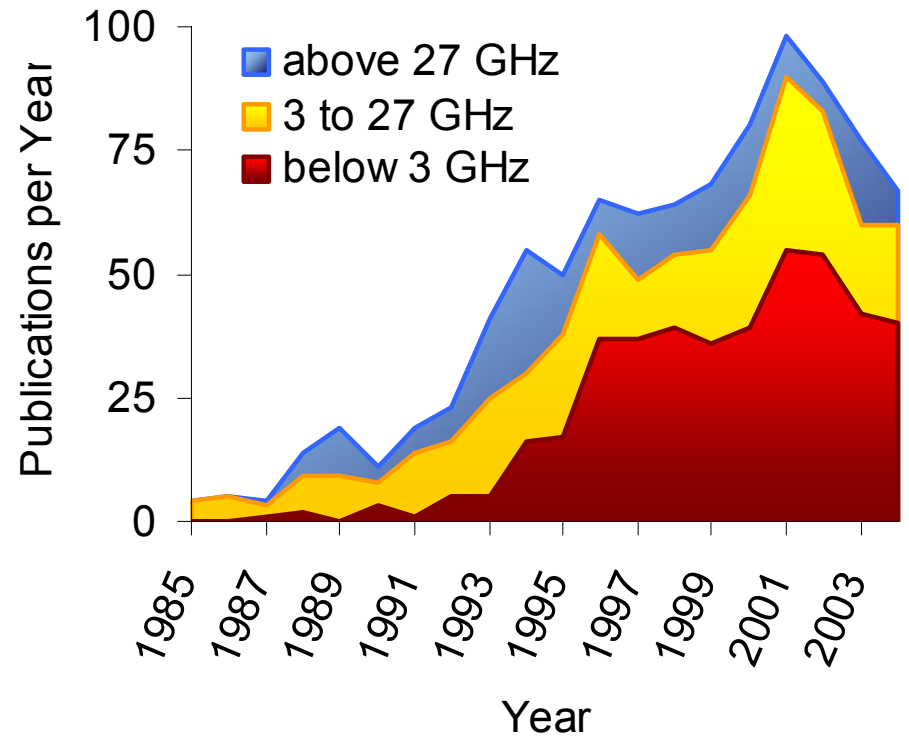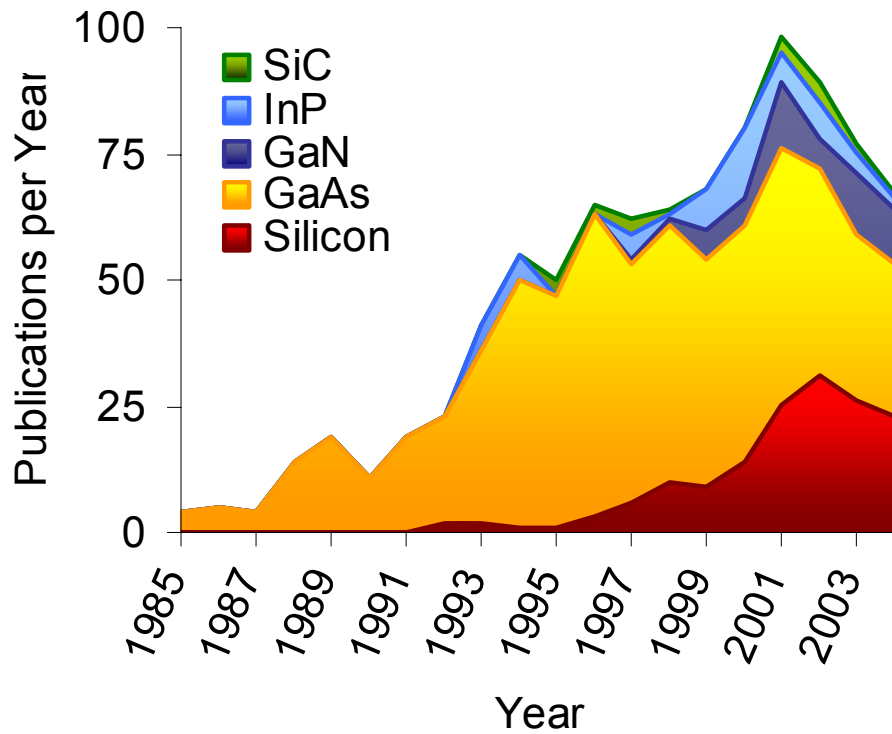Research activity by material and frequency




Compilation of research papers from IEEE Xplore by J. Scholvin

RF power technologies: 1993 vs. 2003

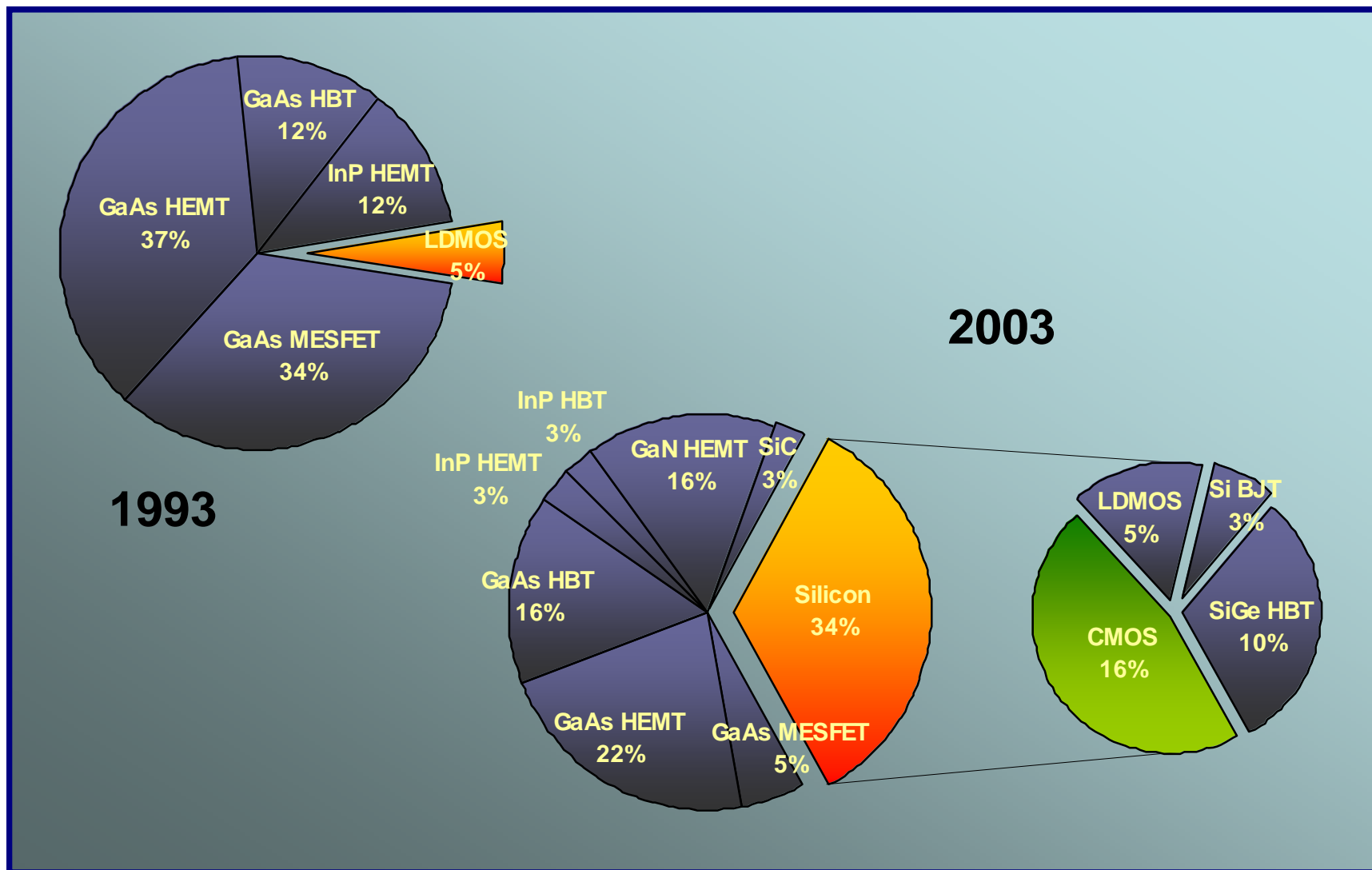


Compilation of research papers from IEEE Xplore by J. Scholvin

RF Power Figures of Merit

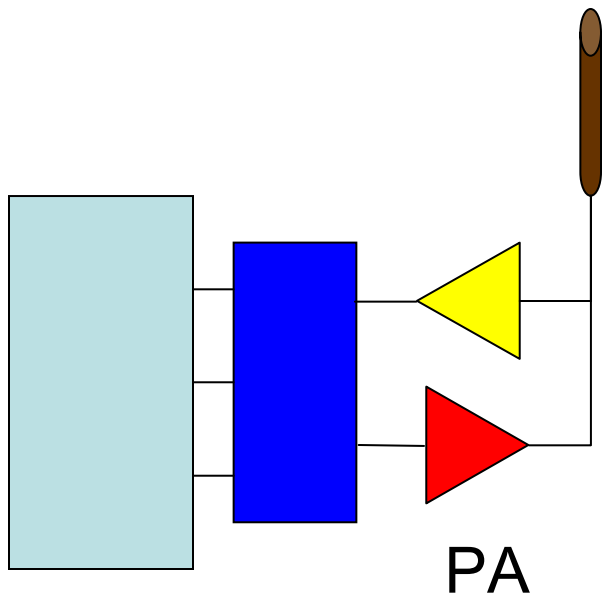


- PA specs:
 - Frequency
 - Power
 - Gain
 - Linearity
 - Voltage
 - Reliability
 - Power efficiency
 - Cost

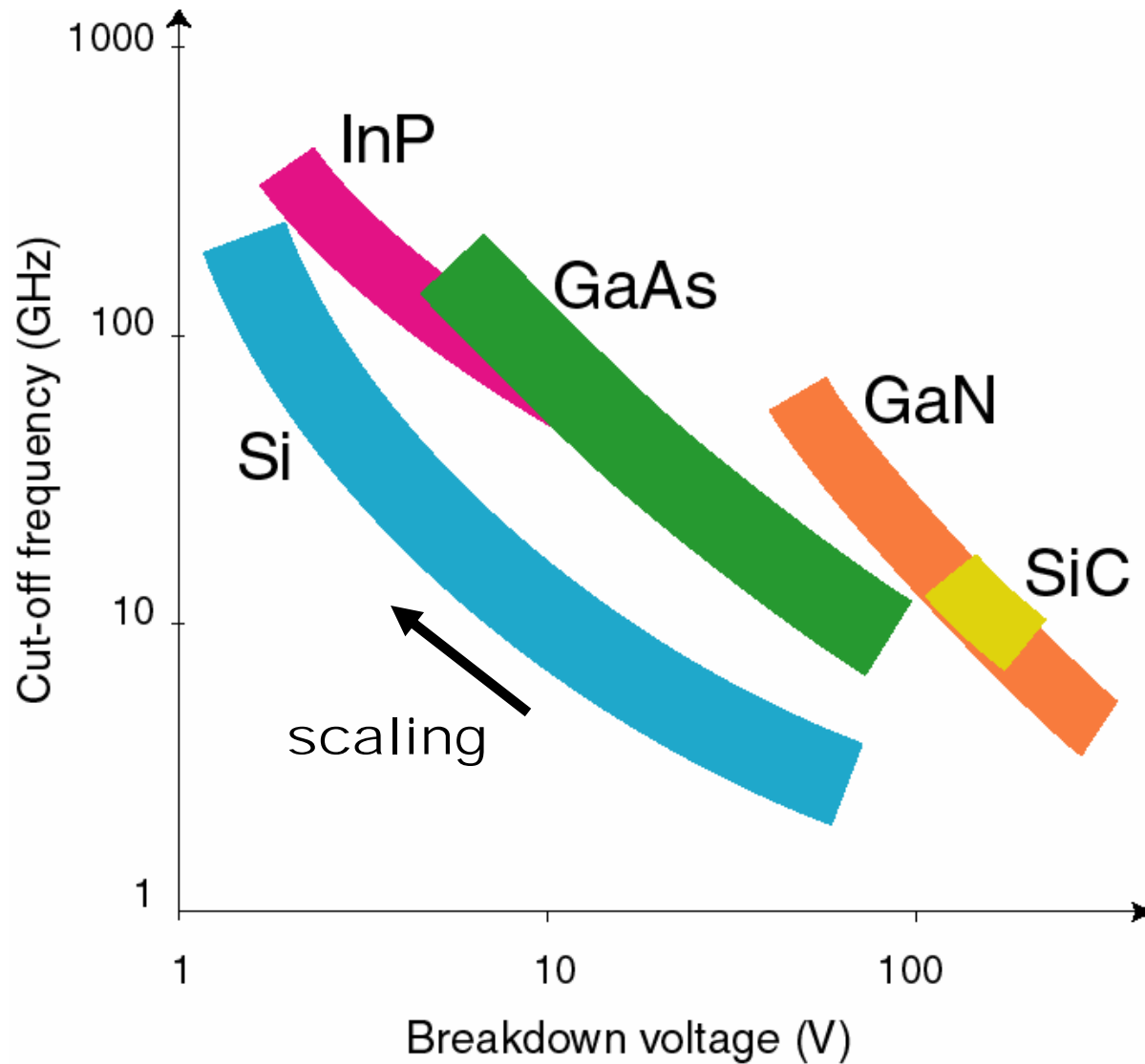
Fundamental trade-off between voltage and frequency



Key to power: supply voltage

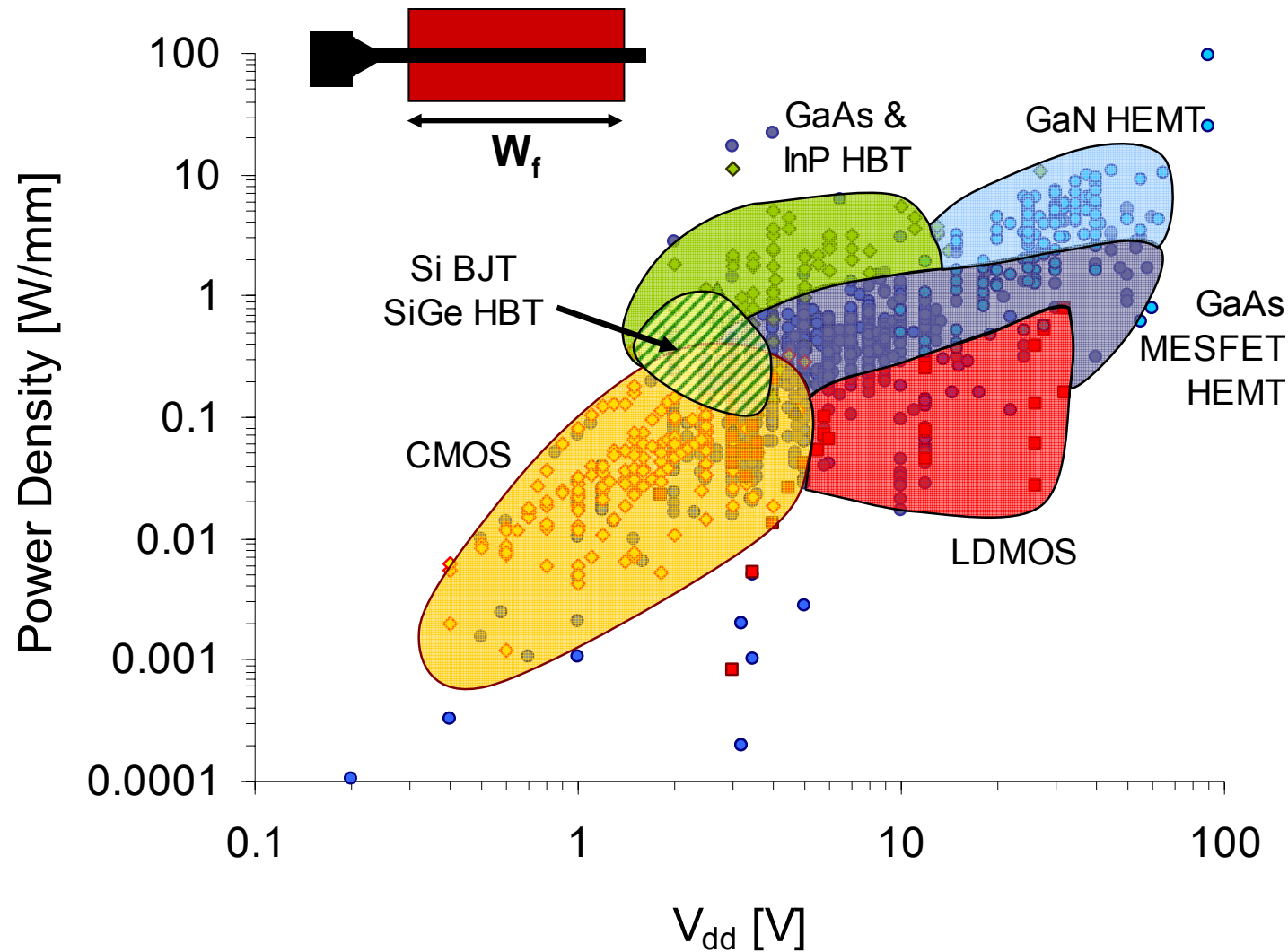


Key to frequency: efficiency

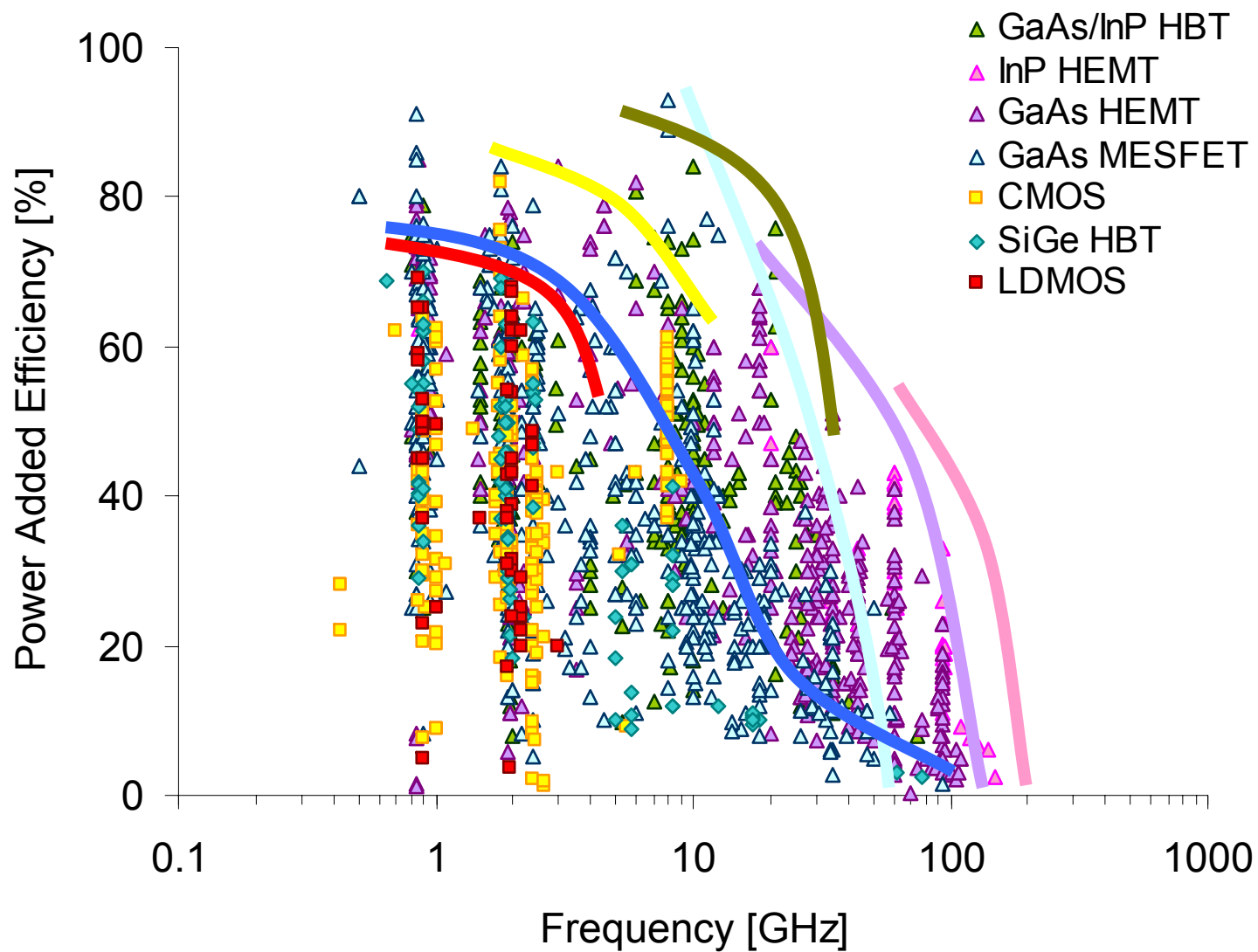


Compilation of research papers from IEEE Xplore by J. Scholvin

The benefits of scaling

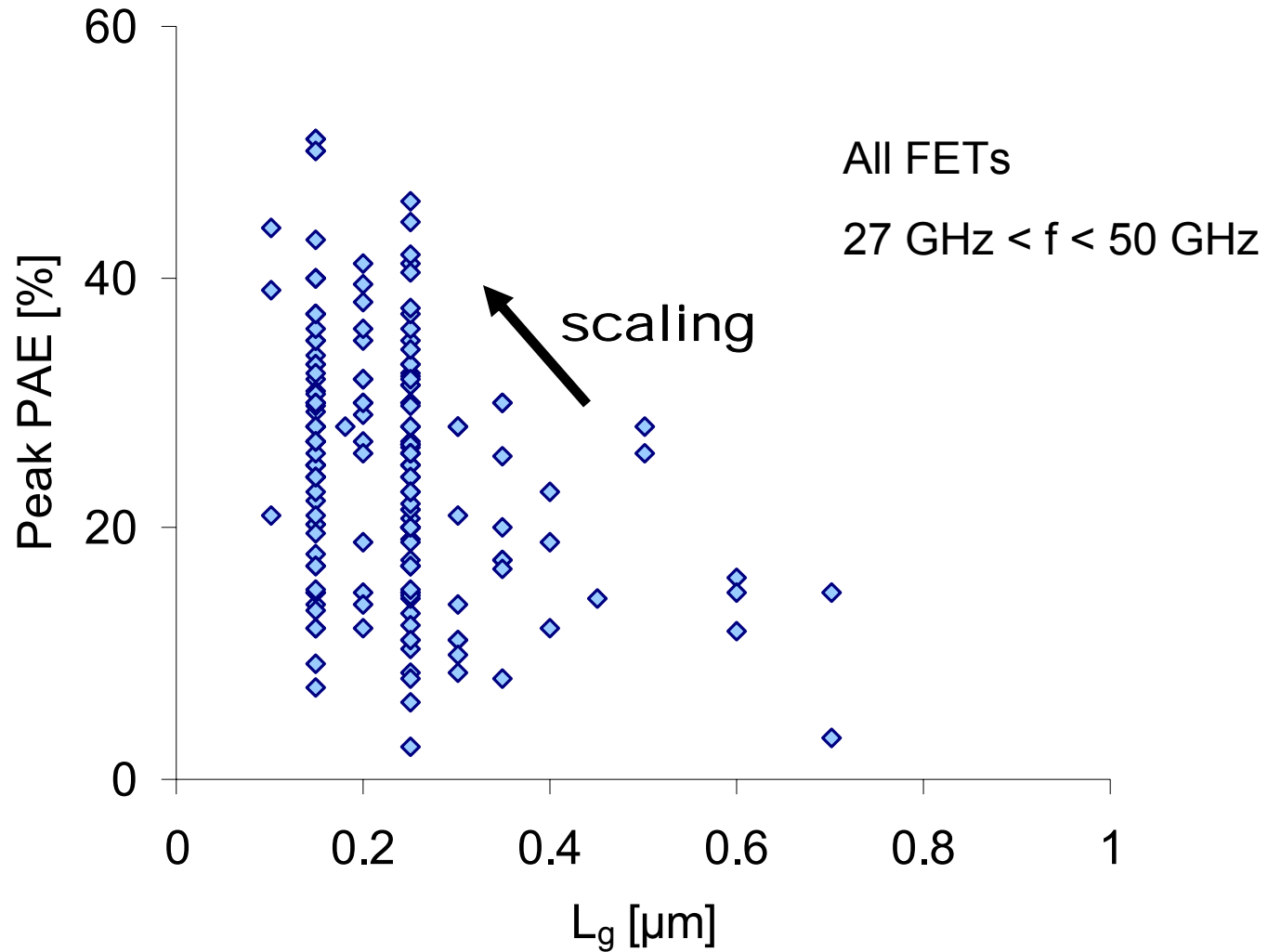

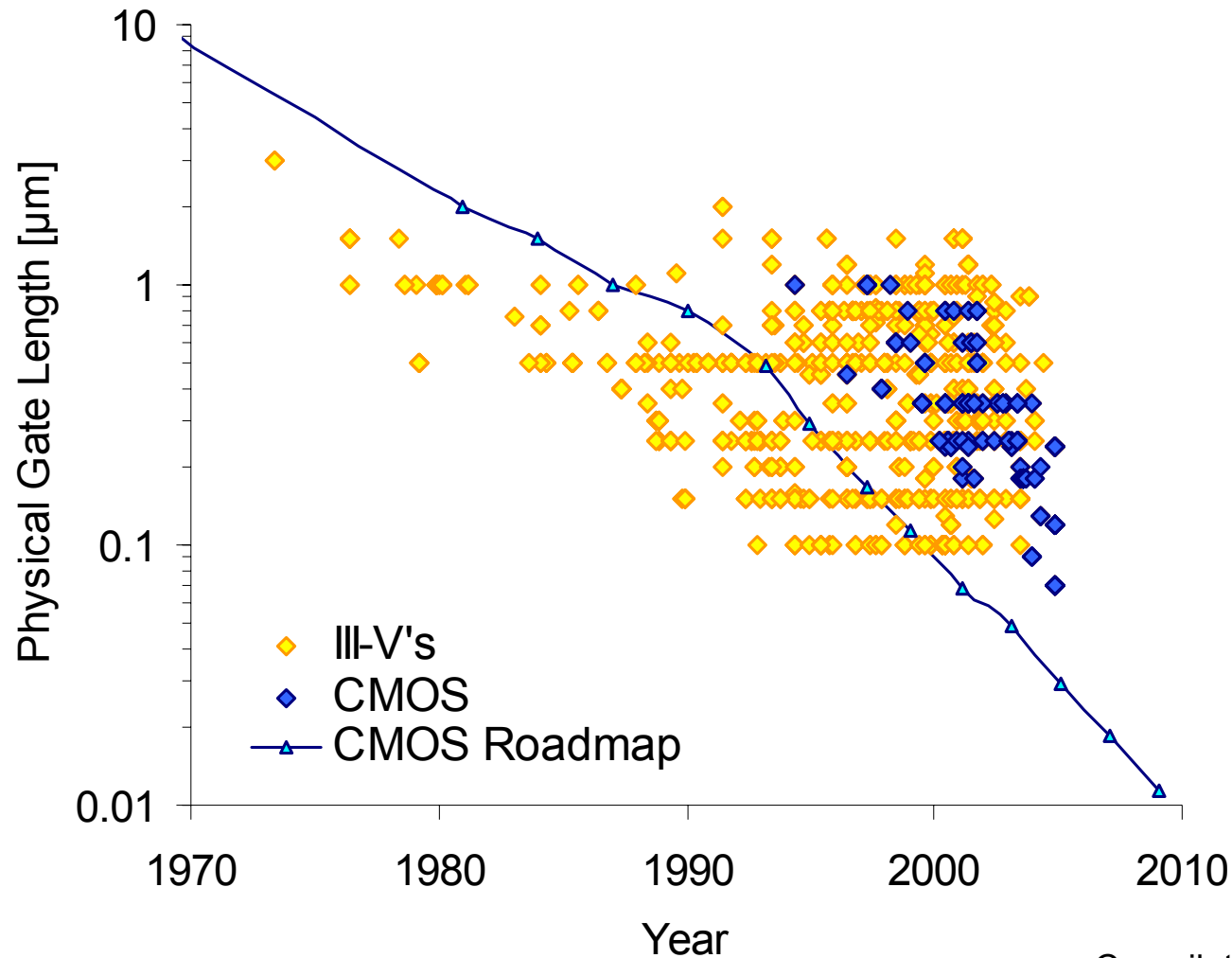
Gate length scaling in III-V FETs and CMOS



Si CMOS: a disruptive technology for RF power?

Compilation of research papers from IEEE Xplore
by J. Scholvin

Si MOSFETs for RF power

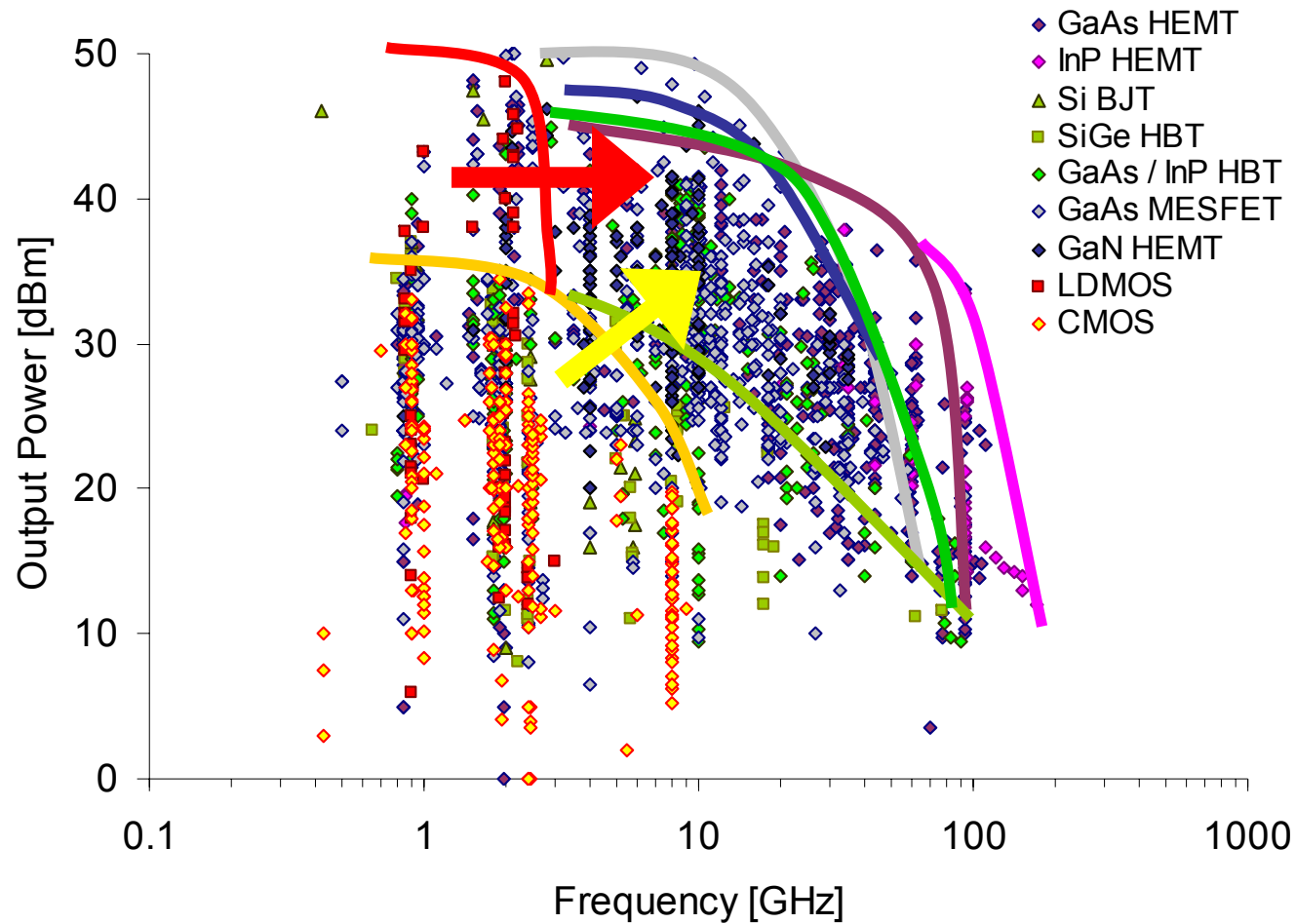


1. Extending LDMOS beyond 2 GHz
2. RF power suitability of deeply scaled CMOS

1. Extending LDMOS beyond 2 GHz


(PhD Thesis of J. Fiorenza)

LDMOSFET: Lightly-doped Drain MOSFET

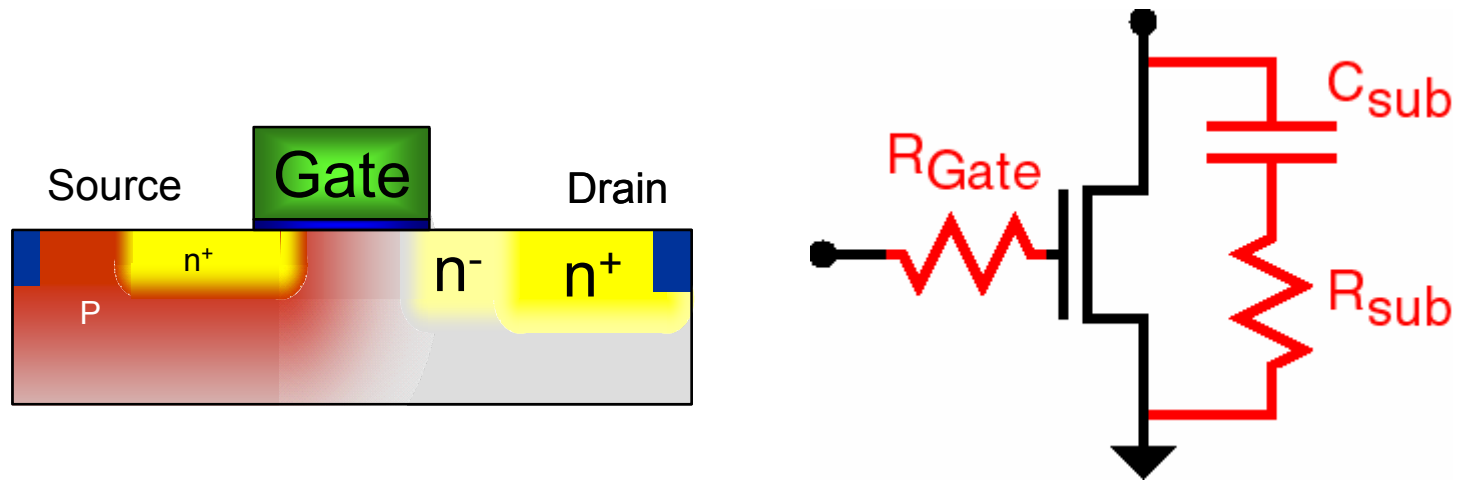

- Two critical sources of RF Loss:
 - Gate resistance loss: reduces power gain
 - Substrate loss: reduces power efficiency

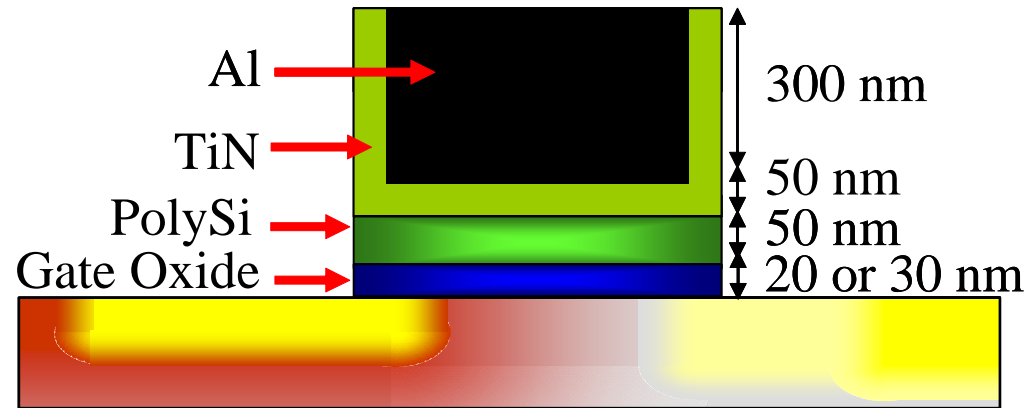Low-loss gate: Metal/Poly-Si damascene gate





Advantages:

- Implemented in the back end of process
- Allows the use of Al or Cu: very low gate resistance
- Self-aligned: no increase in overlap capacitance
- Gate oxide undisturbed

Achieved: 0.2 ohm/sqr (>10 for polySi, ~1 for silic'd gate)

Metal/Poly-Si Damascene Gate

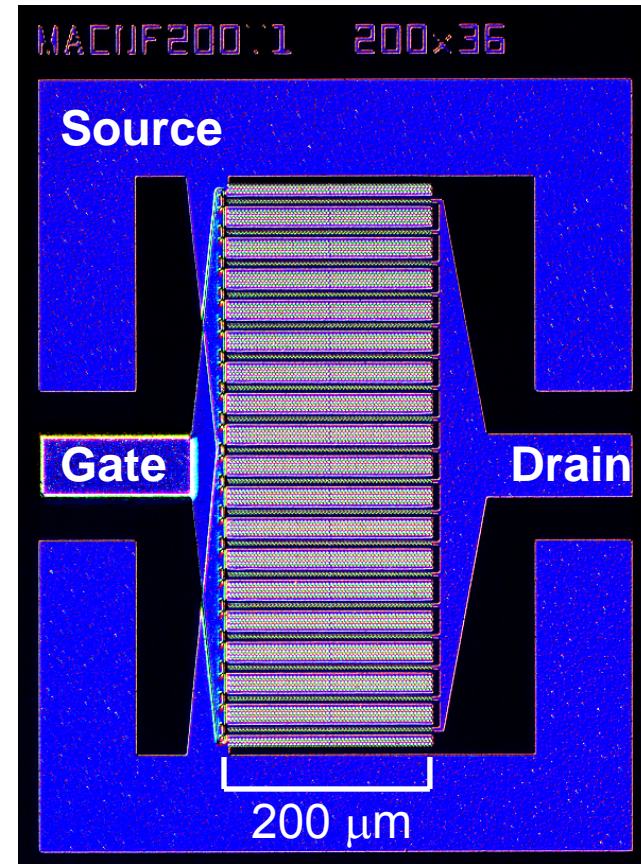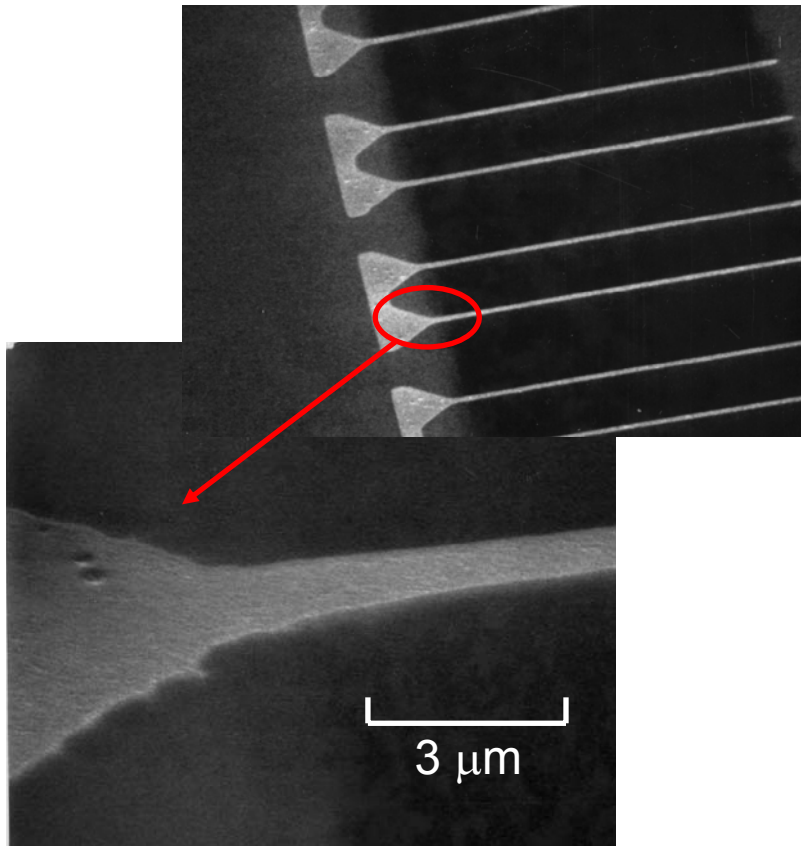

$$L_g = 0.6 \mu\text{m} \quad f_t \sim 15 \text{ GHz} \quad BV_{\text{off}} > 18 \text{ V}$$


Test chip

0.6 μm minimum L_g



10 mask levels

2 levels of metal

Fabricated at MIT

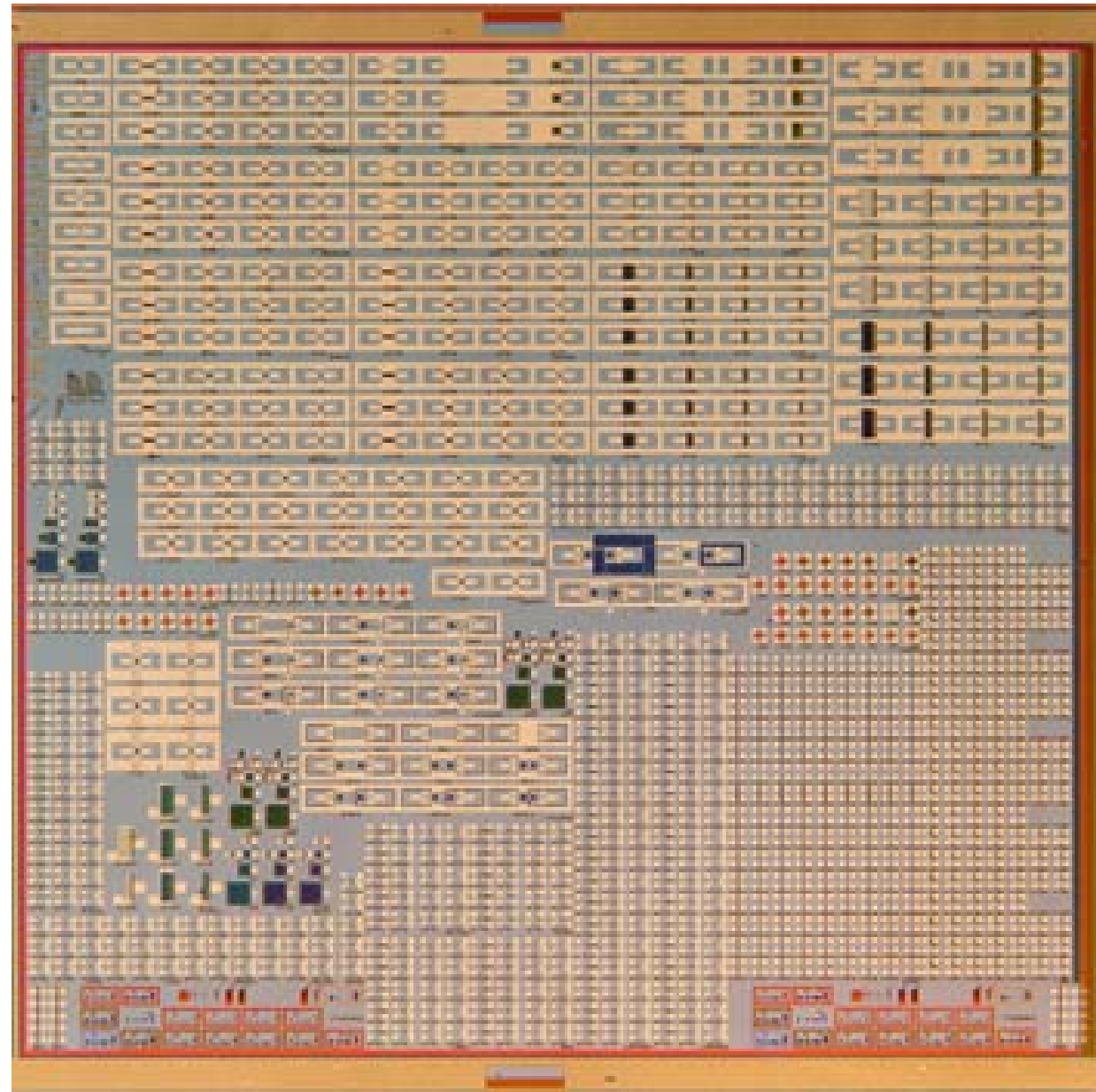


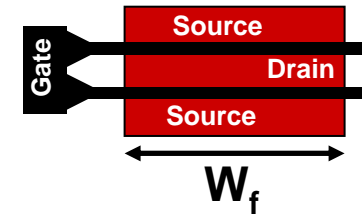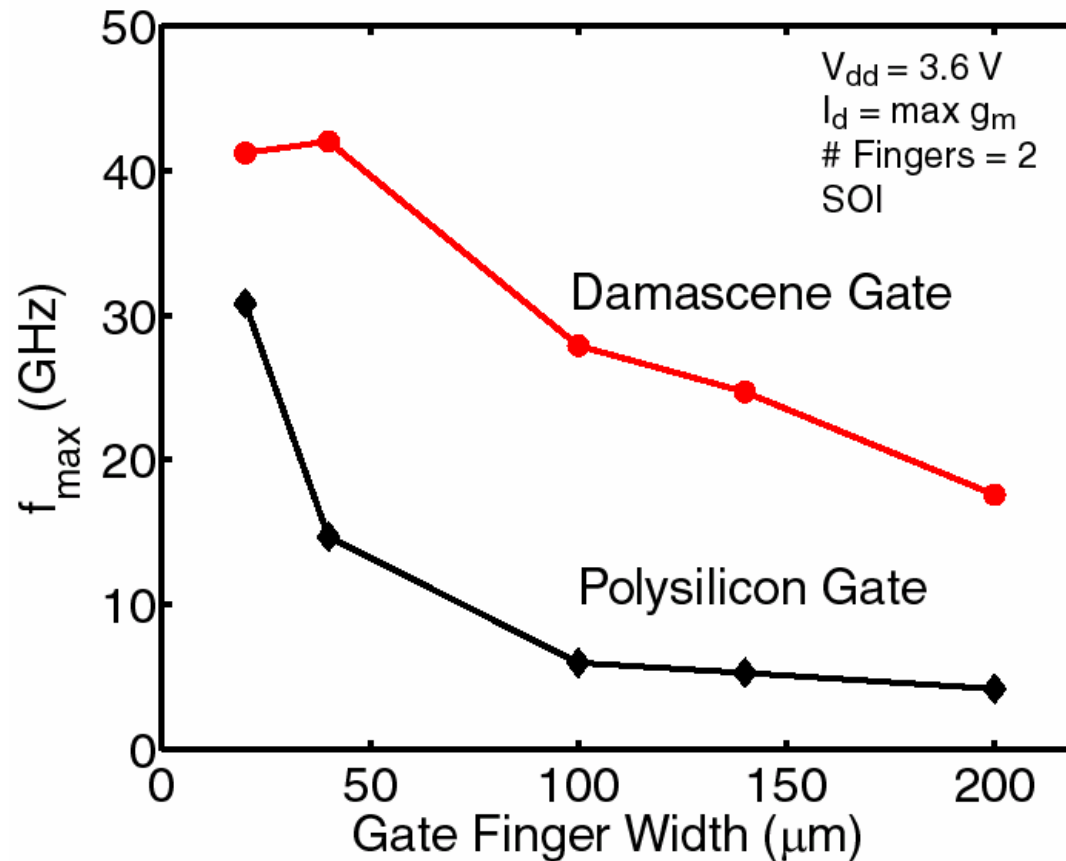Benefit of low gate resistance: small signal




Damascene gate increases f_{\max} , enables wide gate fingers

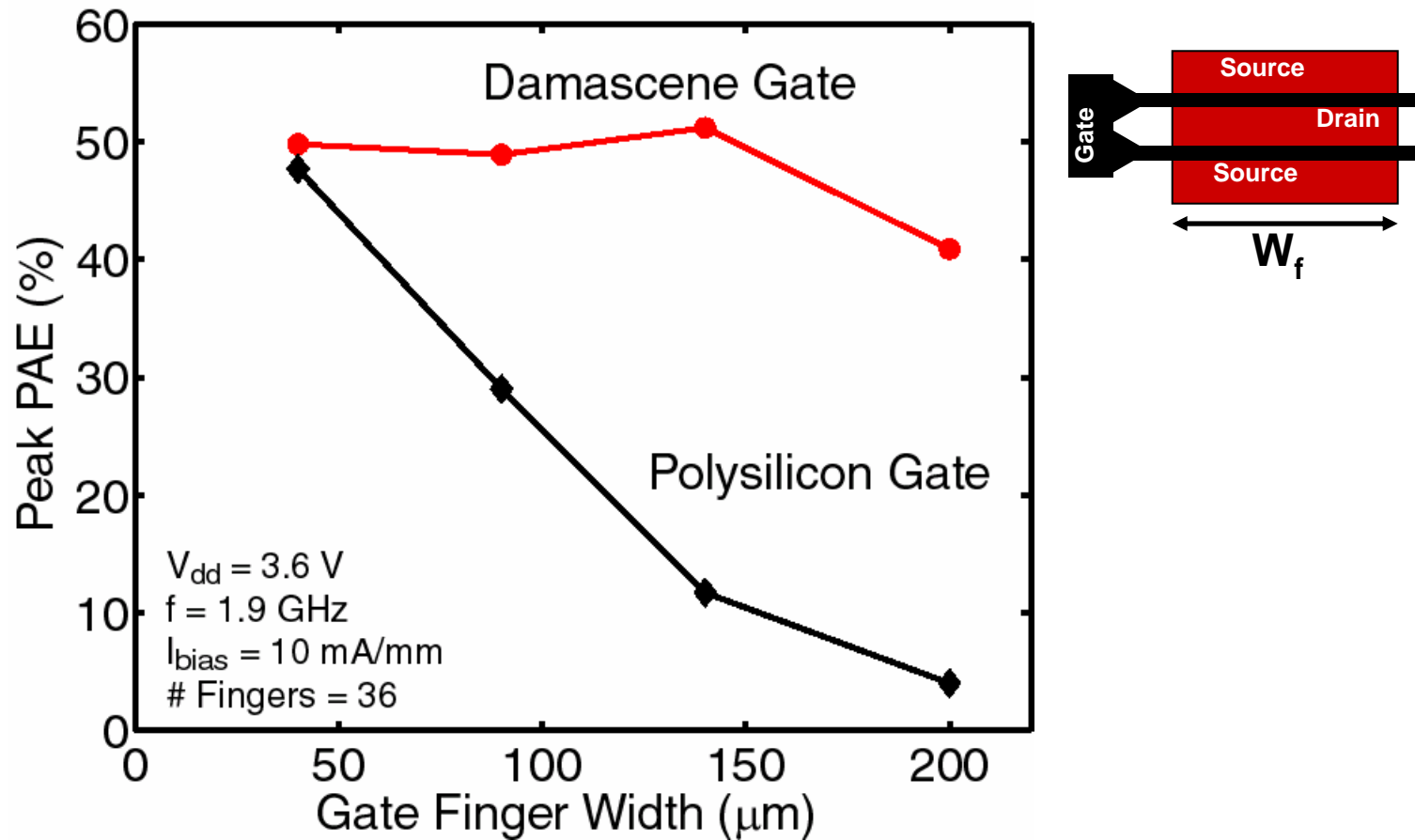Benefit of low gate resistance: large signal



High PAE with gate finger width up to 140 μm

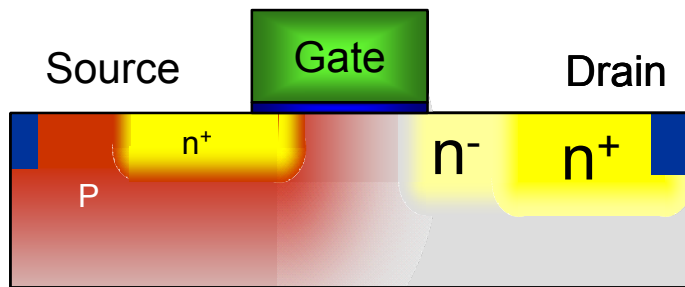
Low-loss substrates: SOI and high-resistivity Si



Bulk Si

Substrate:

- Regular Si
- High-resistivity Si

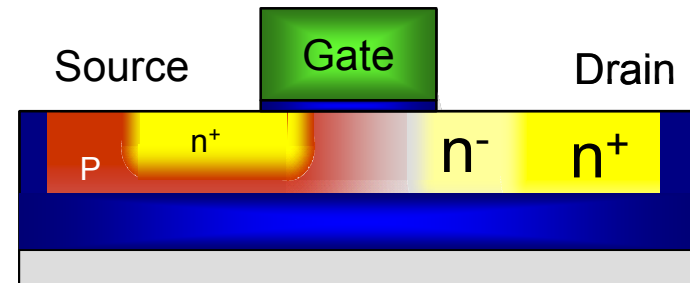


Thin-film SOI

Handle wafer:


- Regular Si
- High-resistivity Si

Impact of substrate

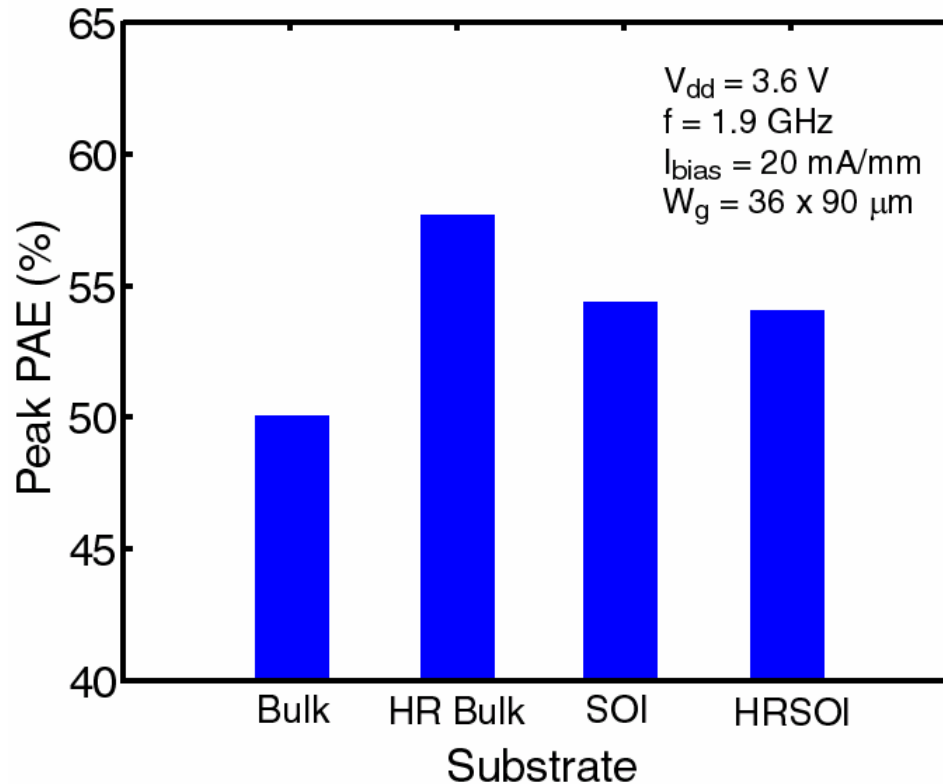



- SOI improves PAE
- High-resistivity silicon improves PAE on bulk
- High-resistivity silicon does not improve PAE on SOI

Beyond 2 GHz

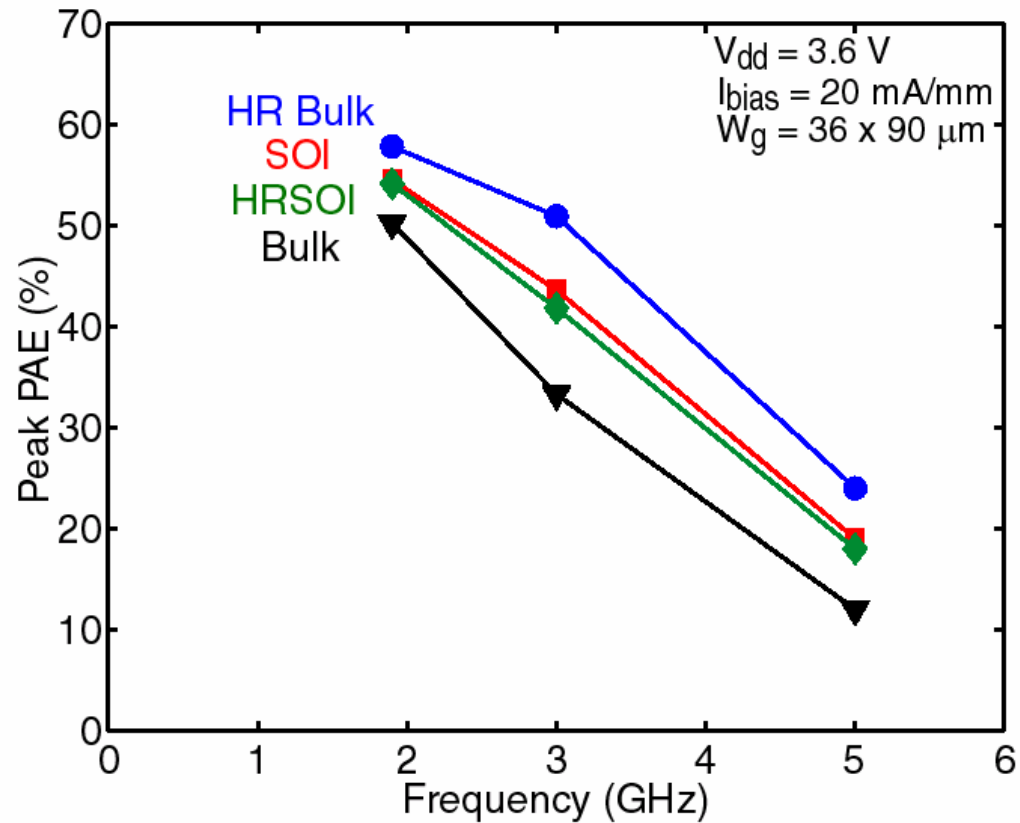

Low-loss substrate very important at high frequencies

Analysis of substrate loss

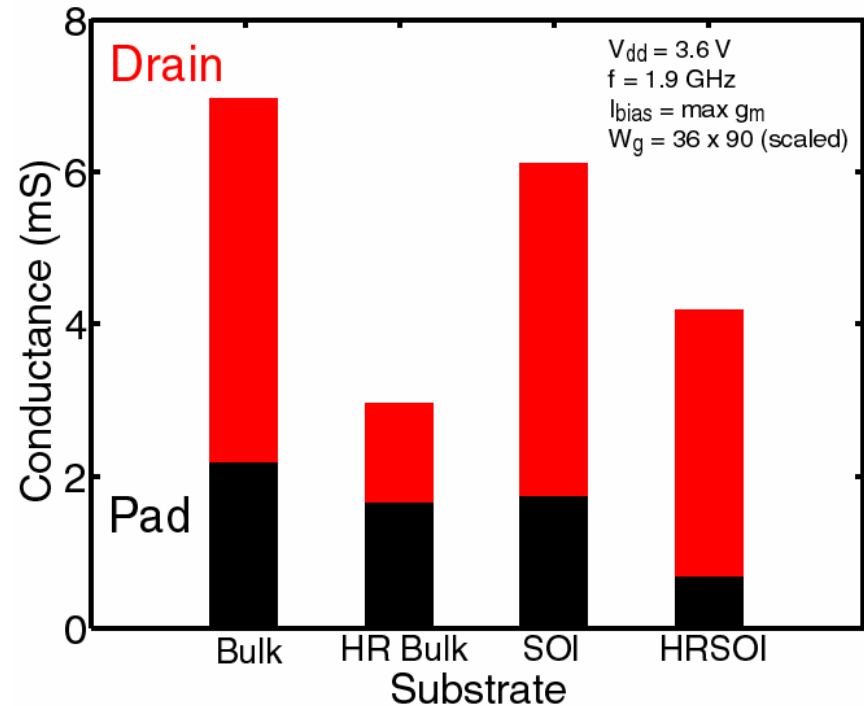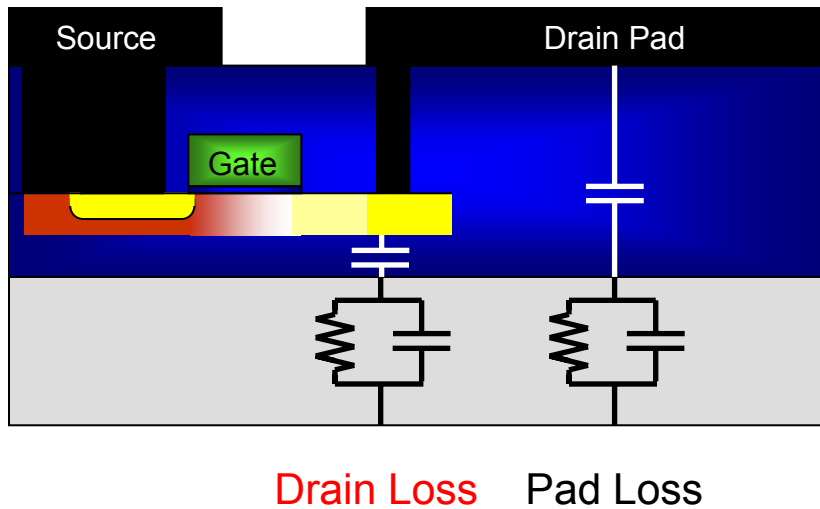


- **Pad Loss:**

- SOI effective
- HR effective on bulk Si and SOI

- **Drain Loss:**



- SOI somehow effective
- HR very effective on bulk Si, only moderately on SOI

Why is HRSOI Ineffective?

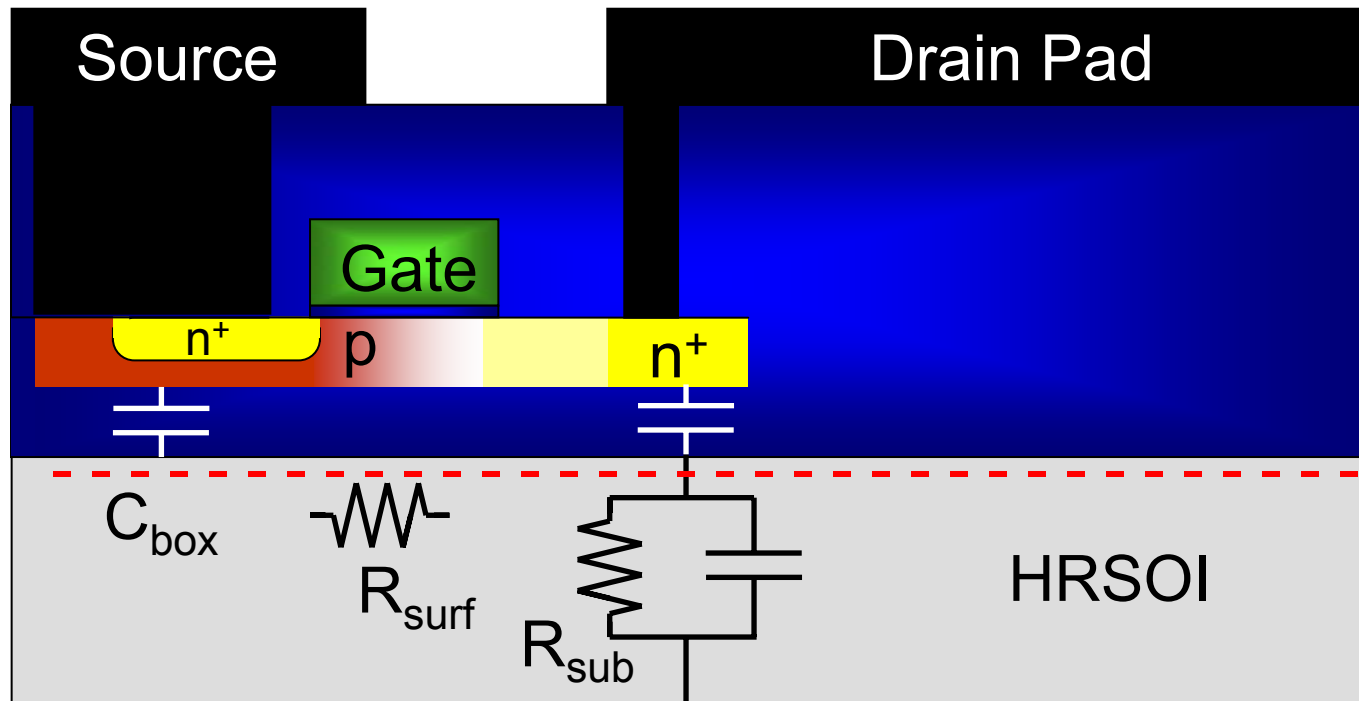


Surface inversion increases drain loss on HRSOI

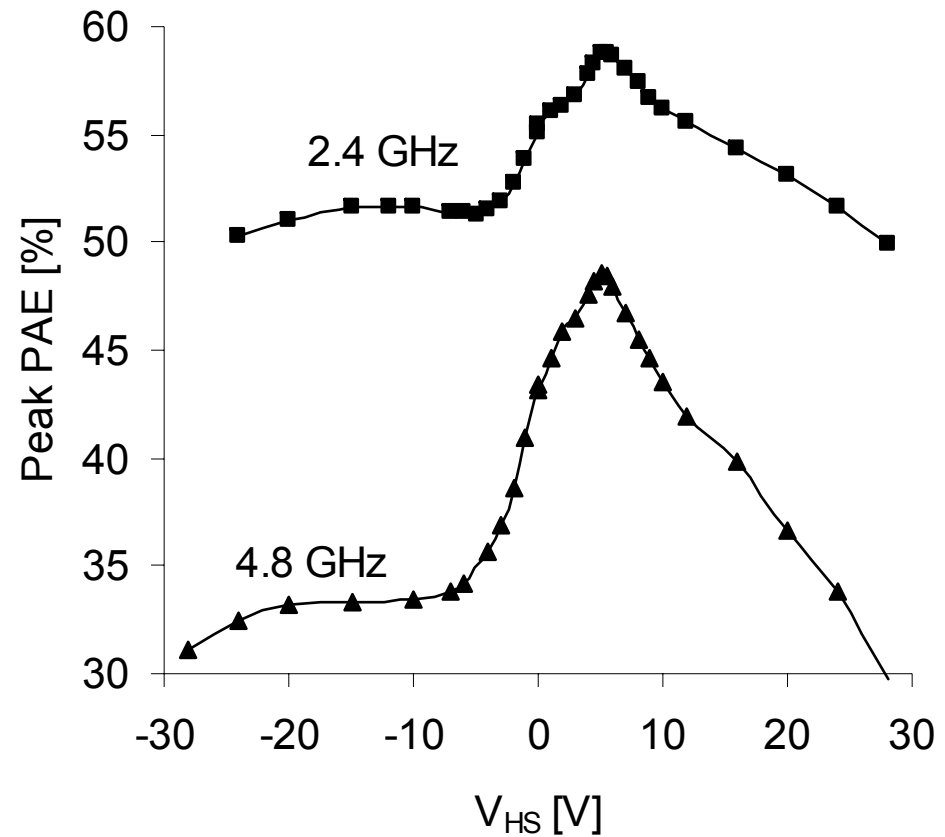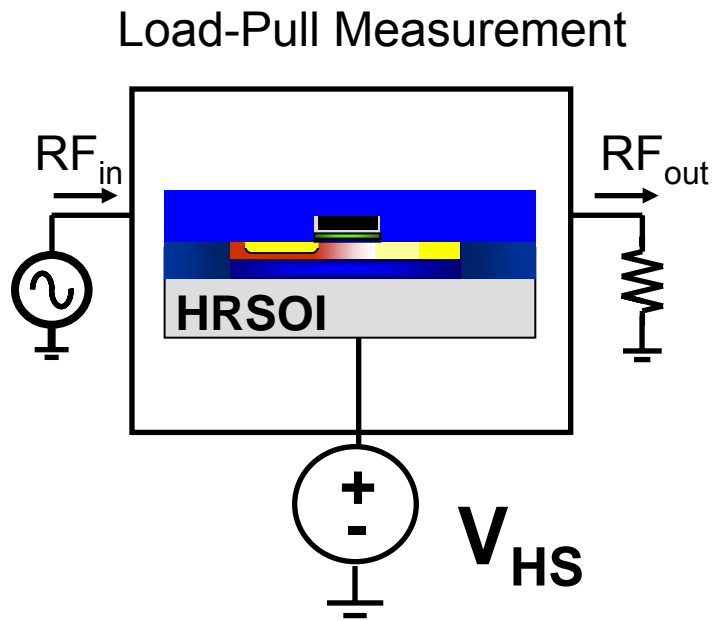Effect of substrate inversion in HRSOI-LDMOS




- Eliminating substrate inversion improves PAE
- Most prominent at high frequencies

Impact of inversion layer elimination

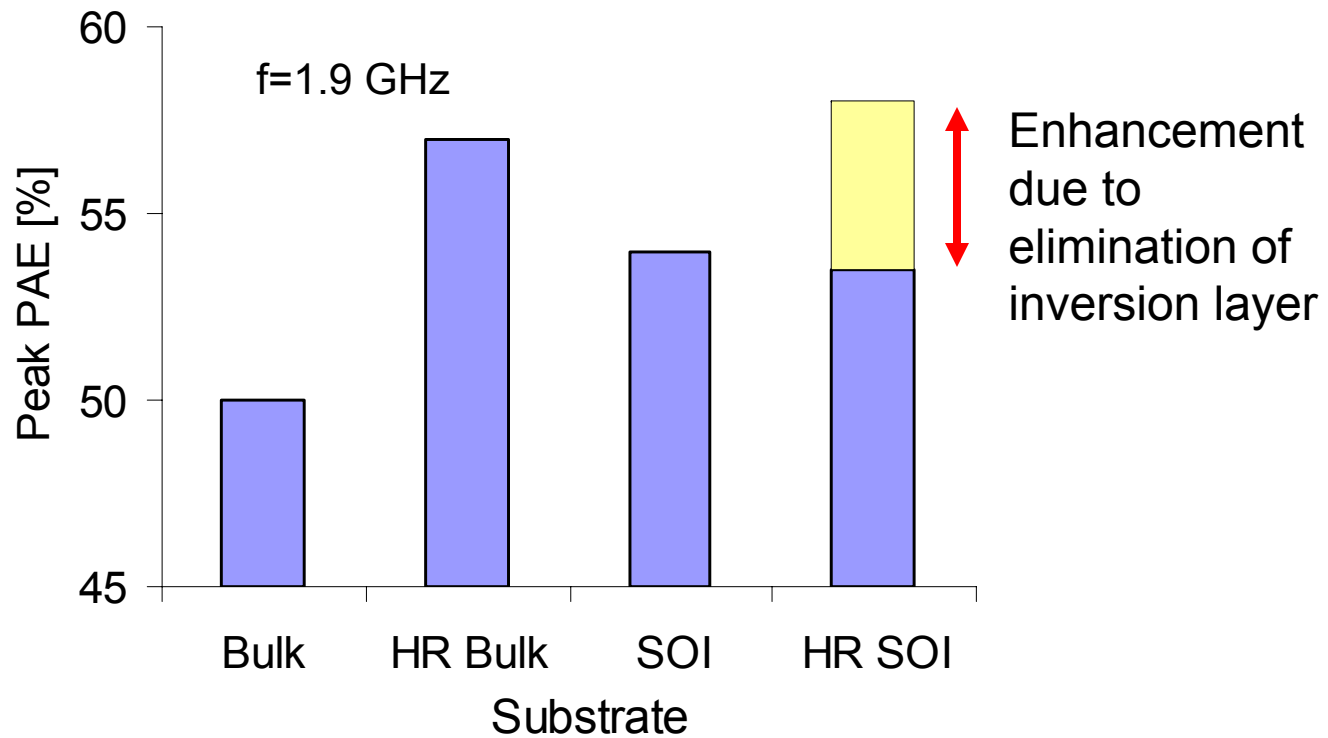


Impact of inversion layer elimination

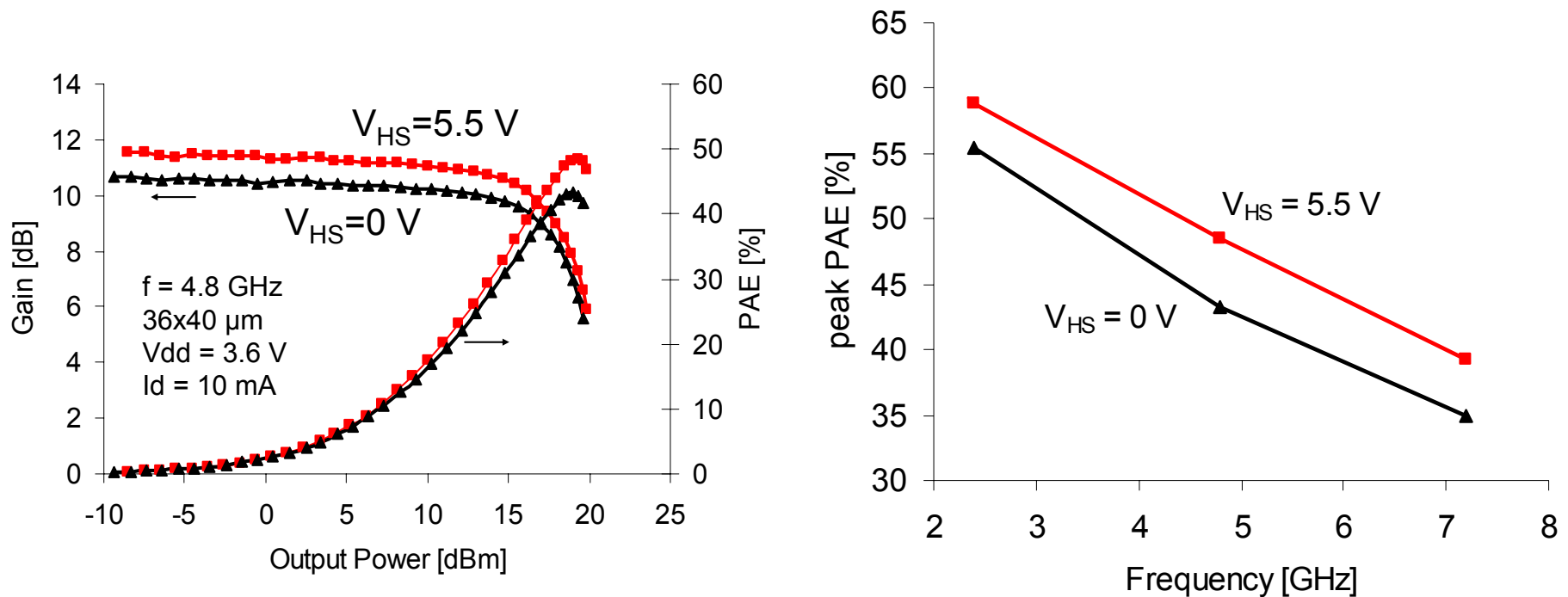- Eliminating substrate surface effects improves performance:
 - Particularly prominent in LDMOS due to large drain area
 - Both linear and saturated performance
 - Most prominent at high frequencies



Si MOSFETs for RF power

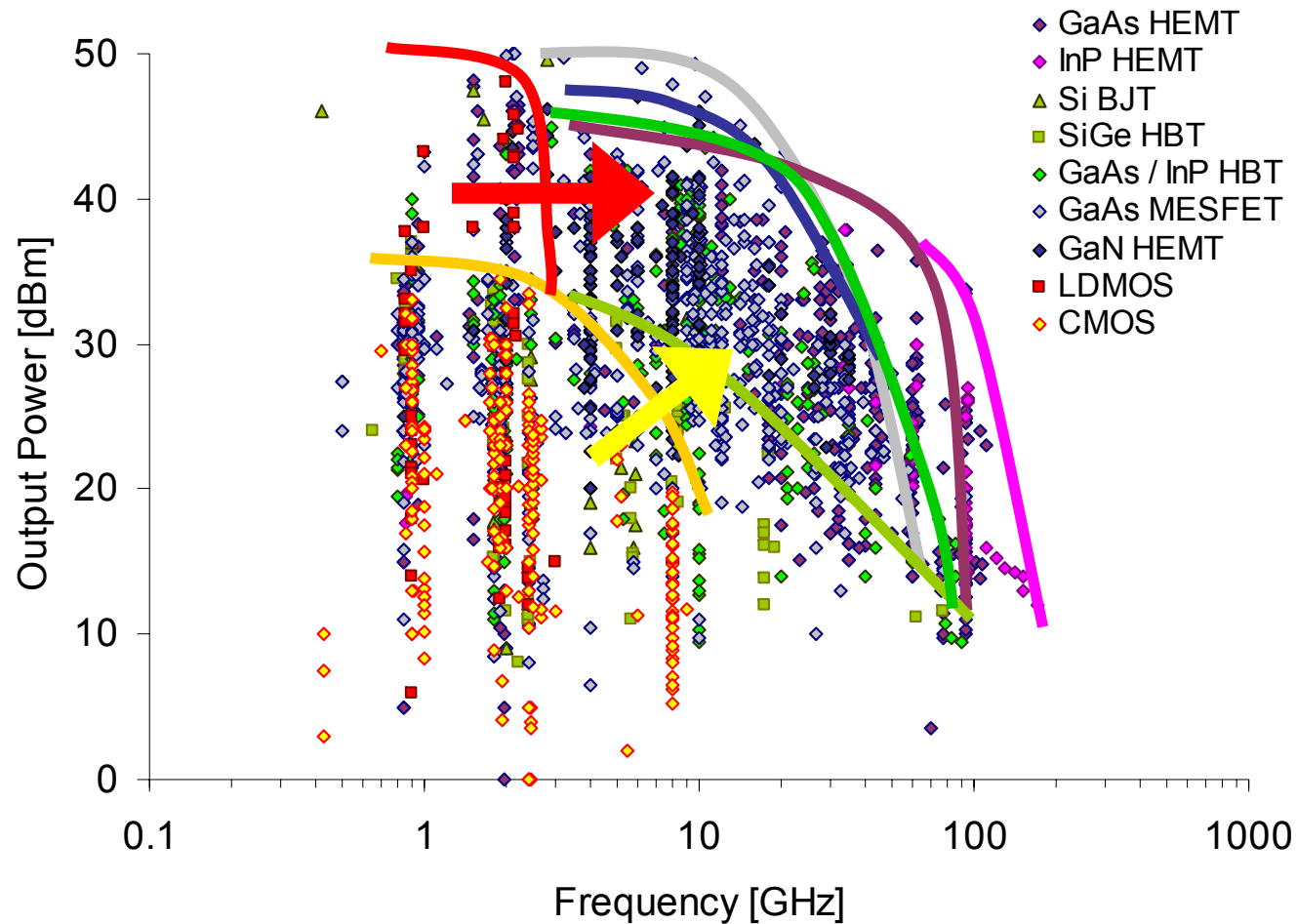

1. Extending LDMOS beyond 2 GHz
2. RF power suitability of deeply scaled CMOS

2. RF power suitability of deeply scaled CMOS


(PhD Thesis of J. Scholvin)

Attractiveness of CMOS:

- System-on-Chip integration
- Low cost
- Low voltage
- Good device models
- Aggressive roadmap
- Wide flavor of devices available

Suitable for:

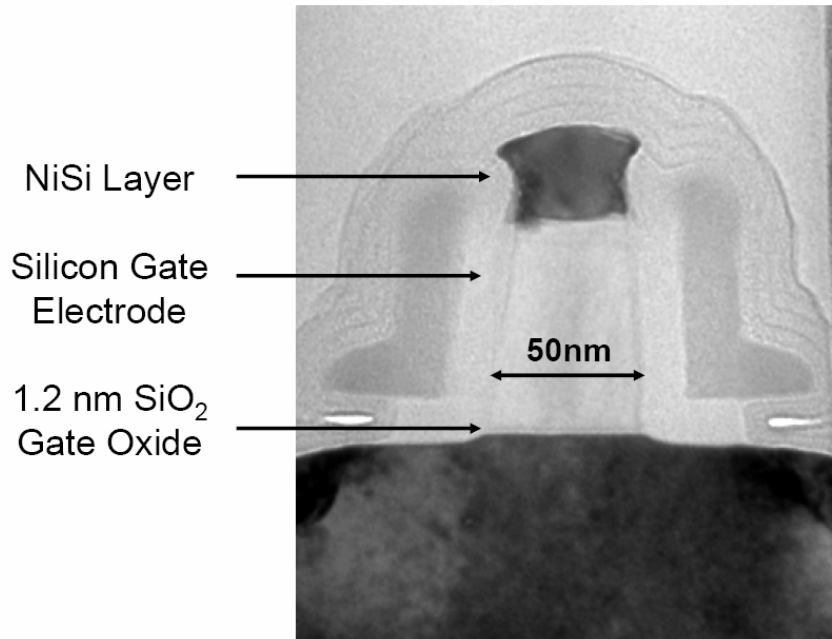- High-volume, low cost consumer ap
- Moderate frequencies (2-10 GHz)
- Medium power (<100 mW)
- Current: WLAN, Bluetooth, Cell-phone PA driver, WiMax/802.16




90 nm CMOS

Picture from:

<http://www.intel.com/research/silicon/micron.htm#silicon>

Issues of CMOS for RF power

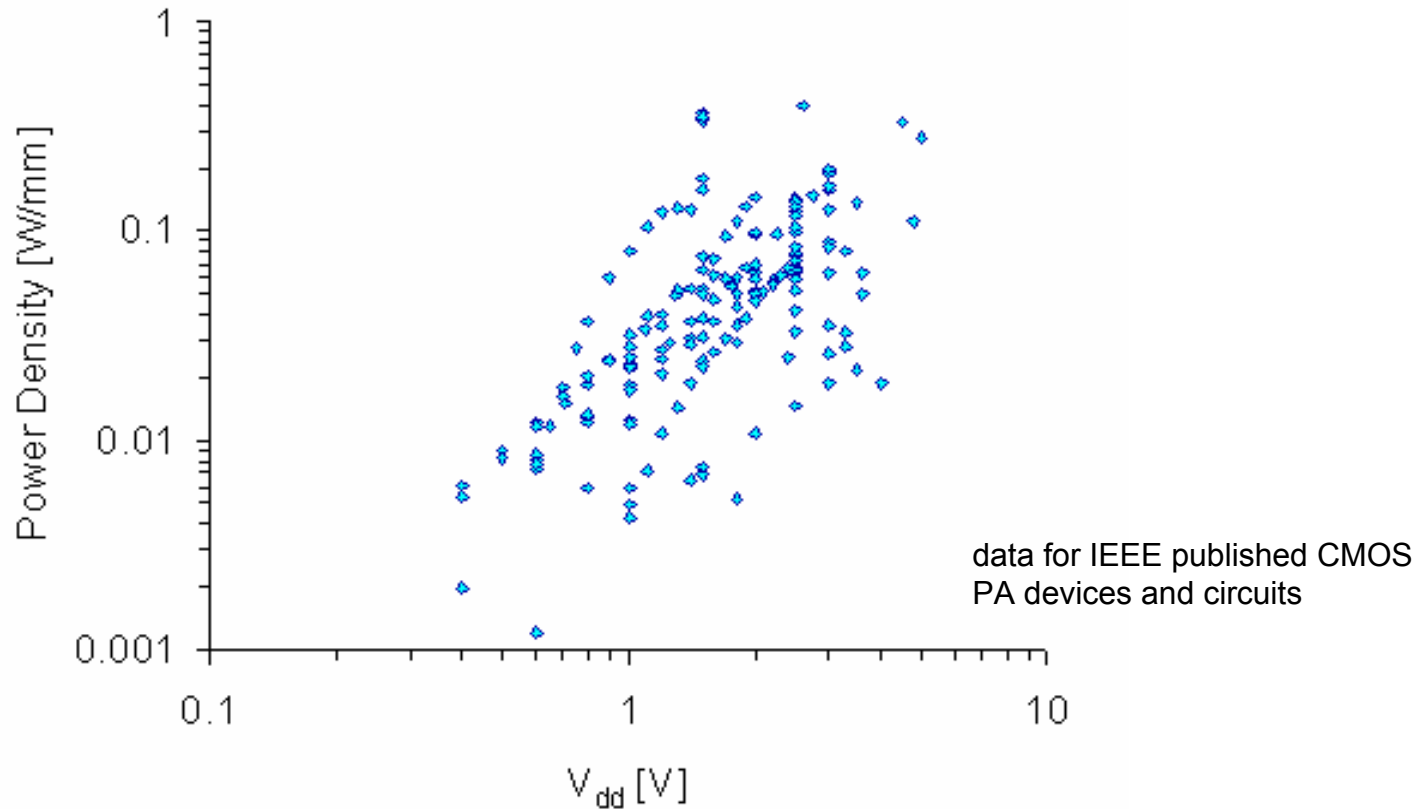- Concerns: CMOS scaling $\Rightarrow V_{dd} \downarrow \Rightarrow P_{out} \downarrow$



- Possible solutions:
 - Raise $V_{dd} \Rightarrow$ impact on reliability
 - Use I/O devices \Rightarrow not really scaling


90 nm CMOS:

there is a lot more than 90 nm devices!

- Includes devices with longer gate lengths and thicker gate oxides for I/O drivers and high V operation
- Designed RF power devices in collaboration with IBM


Oxide thickness	thin (14 Å)	medium (22 Å)	thick (51 Å)
Nominal voltage [V]	1.0	1.2	2.5
$L_g = 90$ nm	X		
$L_g = 130$ nm	X	X	
$L_g = 250$ nm	X	X	X

The benefits of scaling for RF

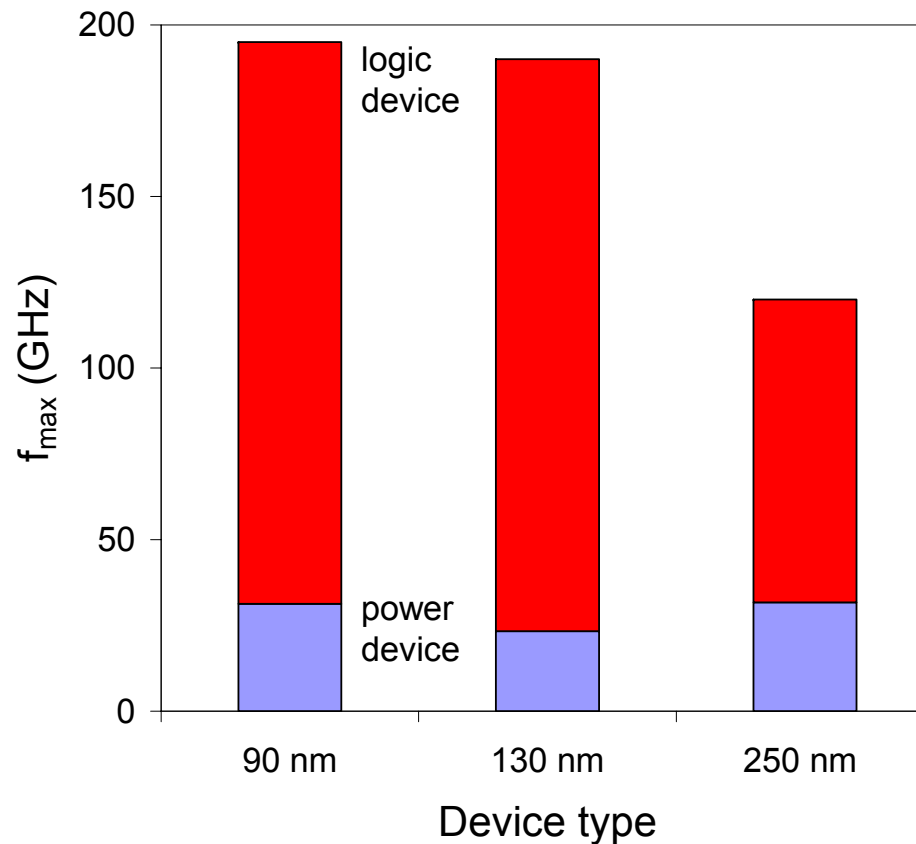


- Logic devices at optimized bias point have very high bandwidth
- But... power devices at class AB bias point have much less bandwidth

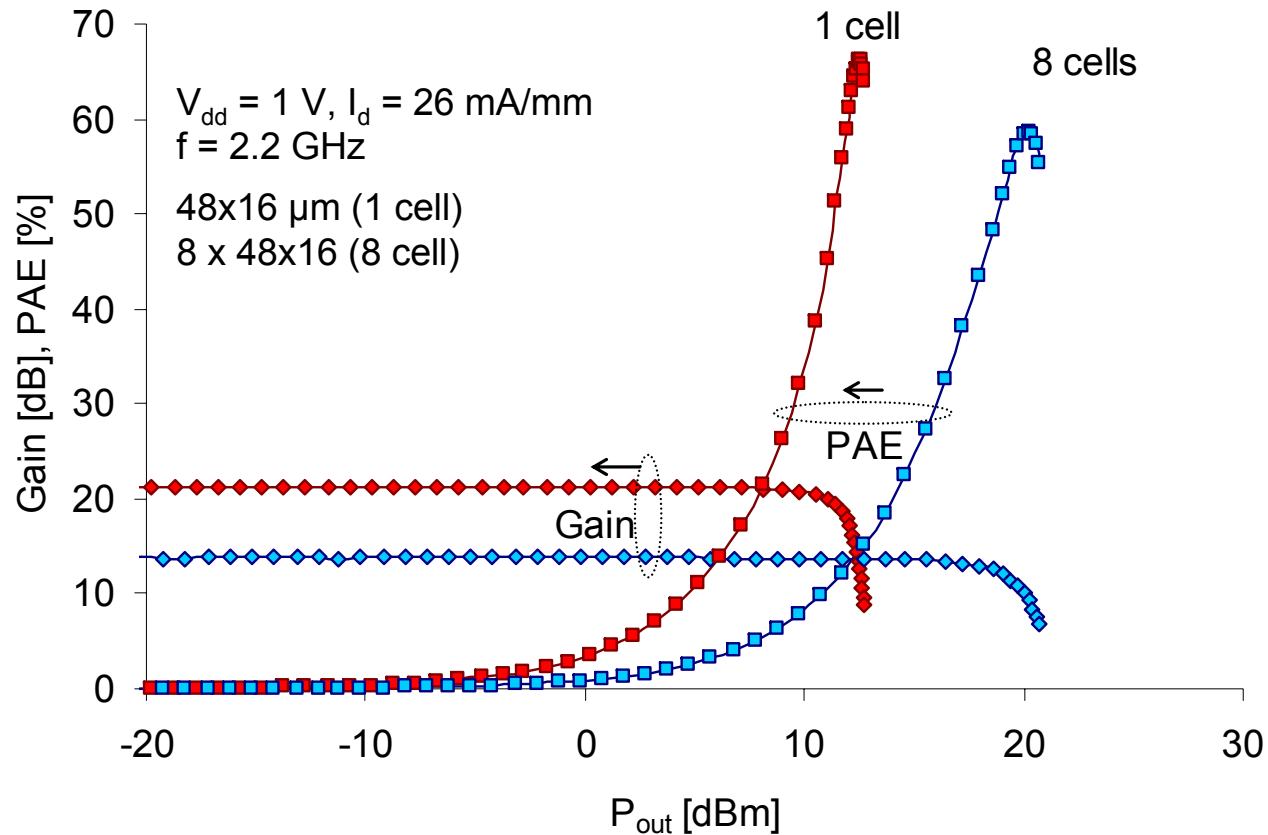RF power performance of standard 90 nm devices




- 1 cell: Peak PAE = 66% at $P_{out} = 12.5 \text{ dBm}$
- 8 cell: Peak PAE = 59% at $P_{out} = 20.2 \text{ dBm}$

Linear performance of 90 nm CMOS

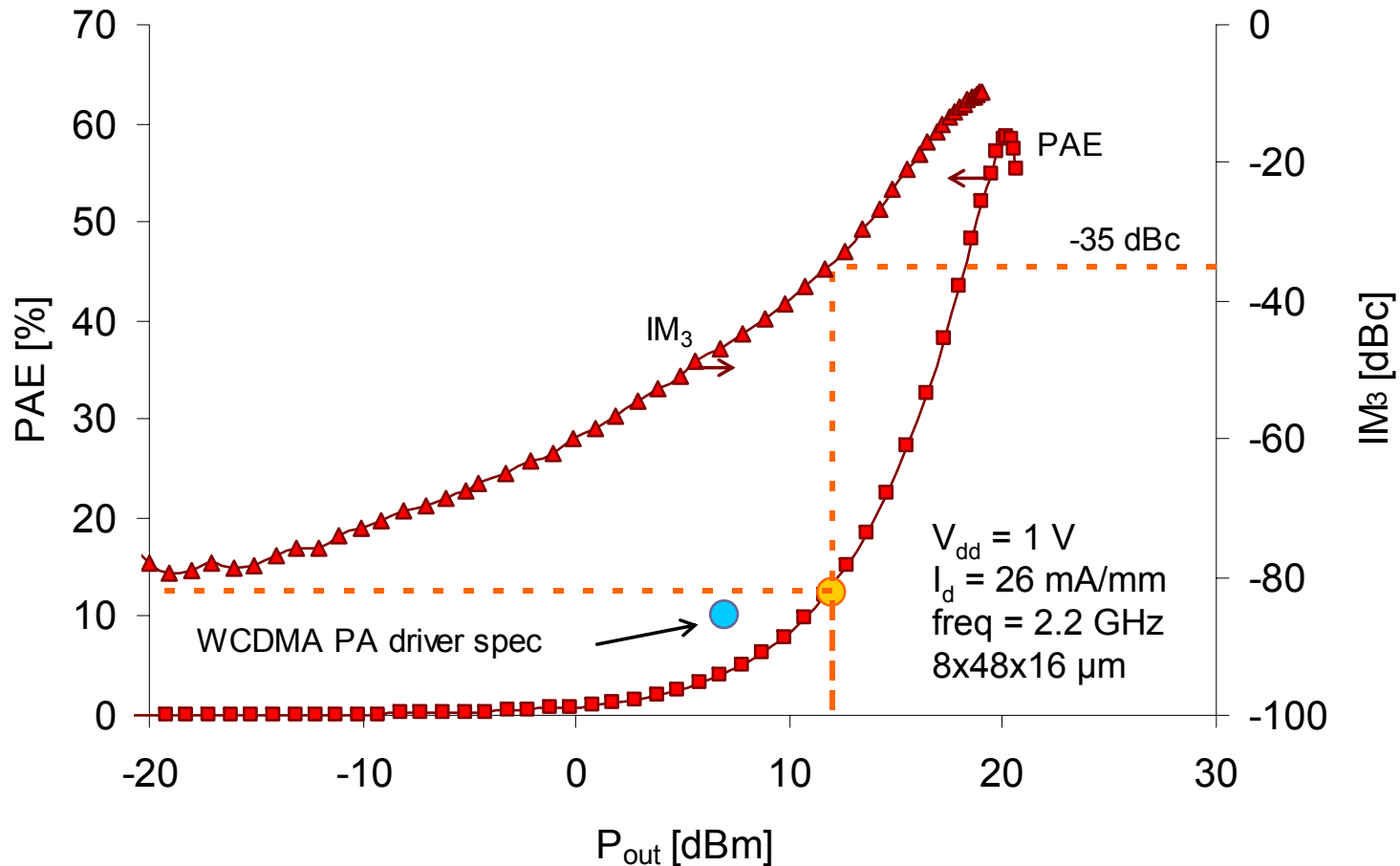



- What is PAE at a given IM_3 ?
 - at $IM_3 = -35$ dBc, PAE = 12% at $P_{out} = 12$ dBm
- Exceeds WCDMA PA driver specs

90 nm vs. 250 nm devices at 8 GHz

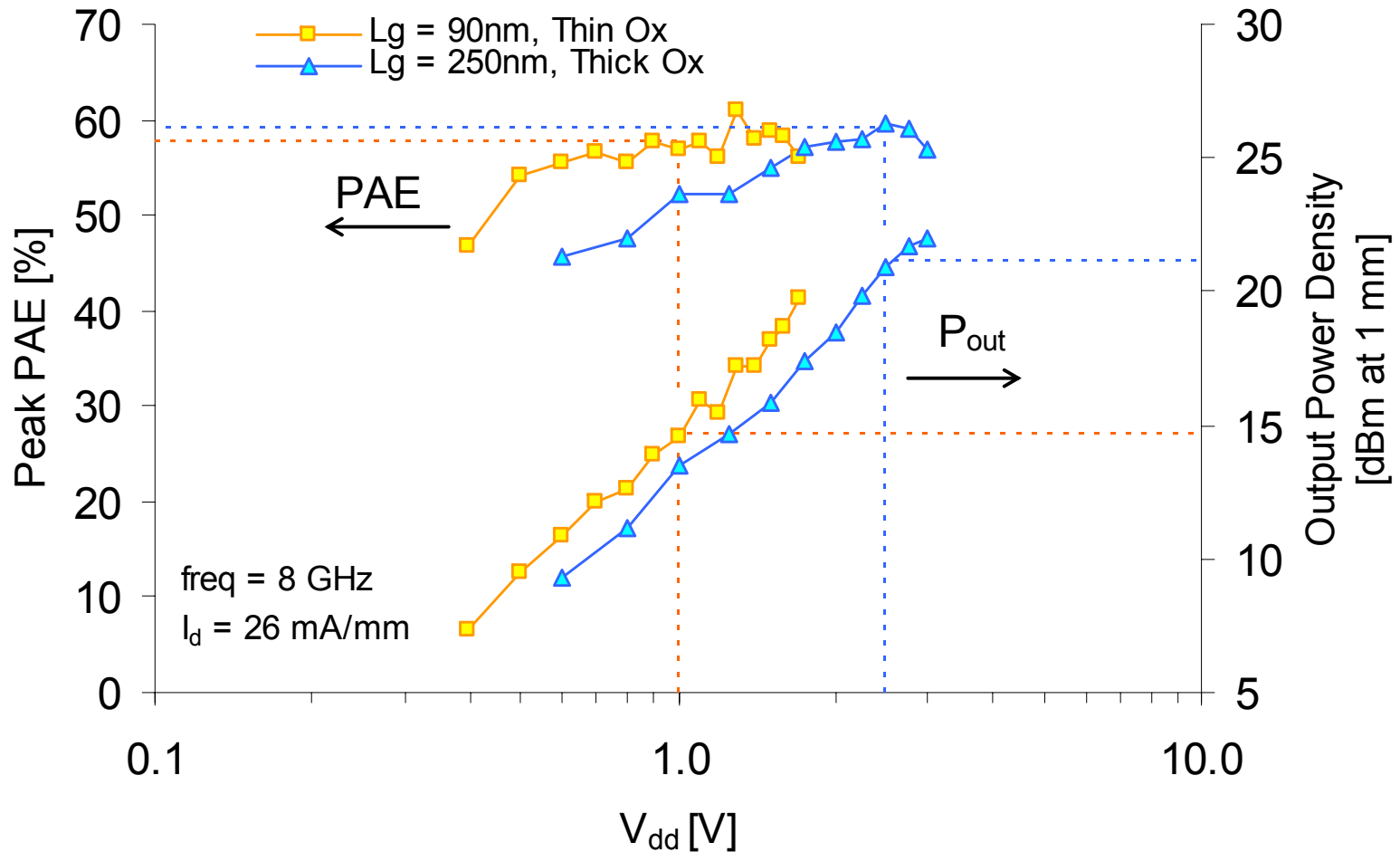

- At $V_{dd} = 1$ V, 90 nm has best PAE and P_{out}
- 250 nm device offers highest power density at $V_{dd} = 2.5$ V

90 nm vs. 250 nm

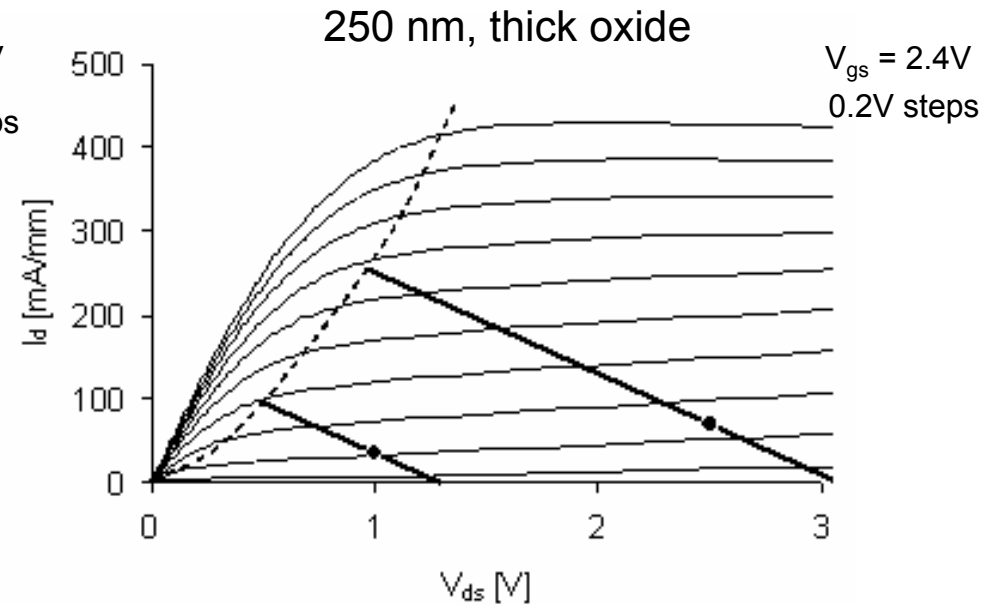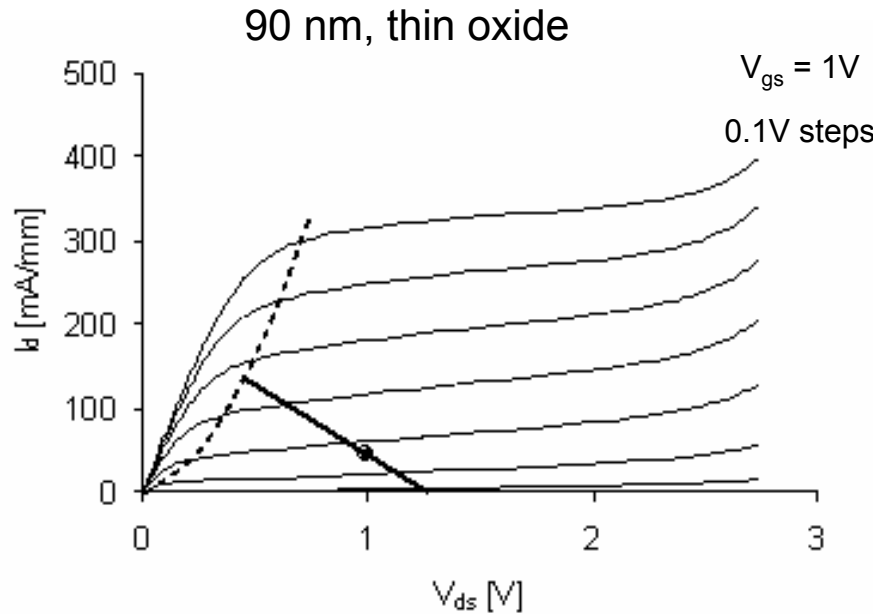


- 250 nm thick oxide device has higher $V_{ds,sat}$
⇒ compresses earlier and softer ⇒ lower P_{out} and peak PAE
- As $V_{dd} \uparrow$ impact of $V_{ds,sat}$ decreases

What about reliability?

For RF power, reliability related to ratio of:


- nominal V_{dd}
- to breakdown voltage

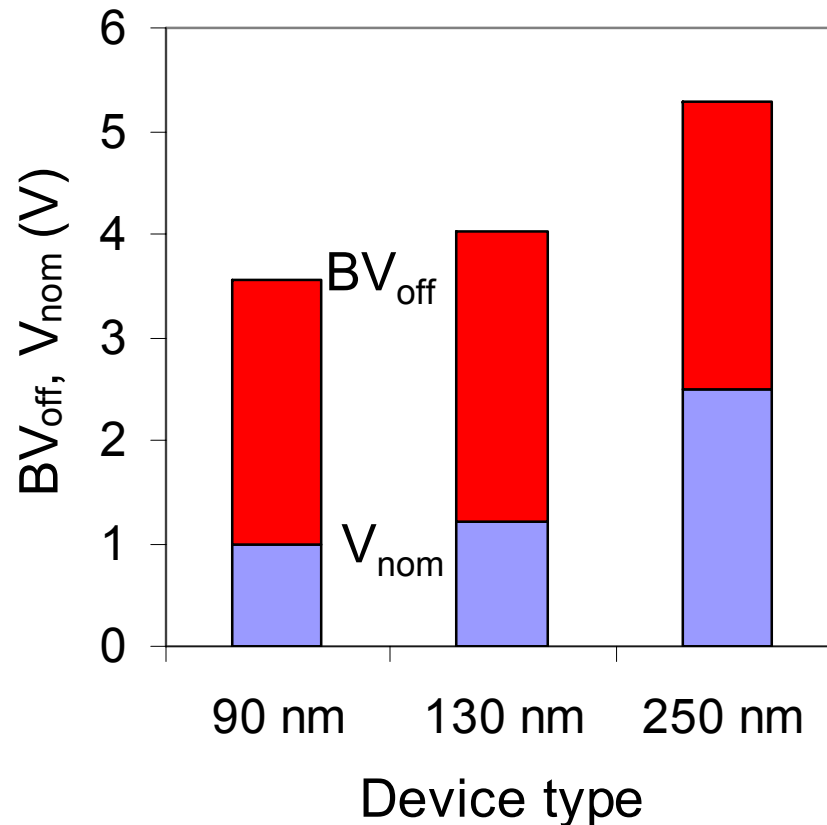

For RF power:


- 90 nm device expected to be **more** reliable at $V_{dd}=1$ V than 250 nm device at 2.5 V

Reliability: impact of output power

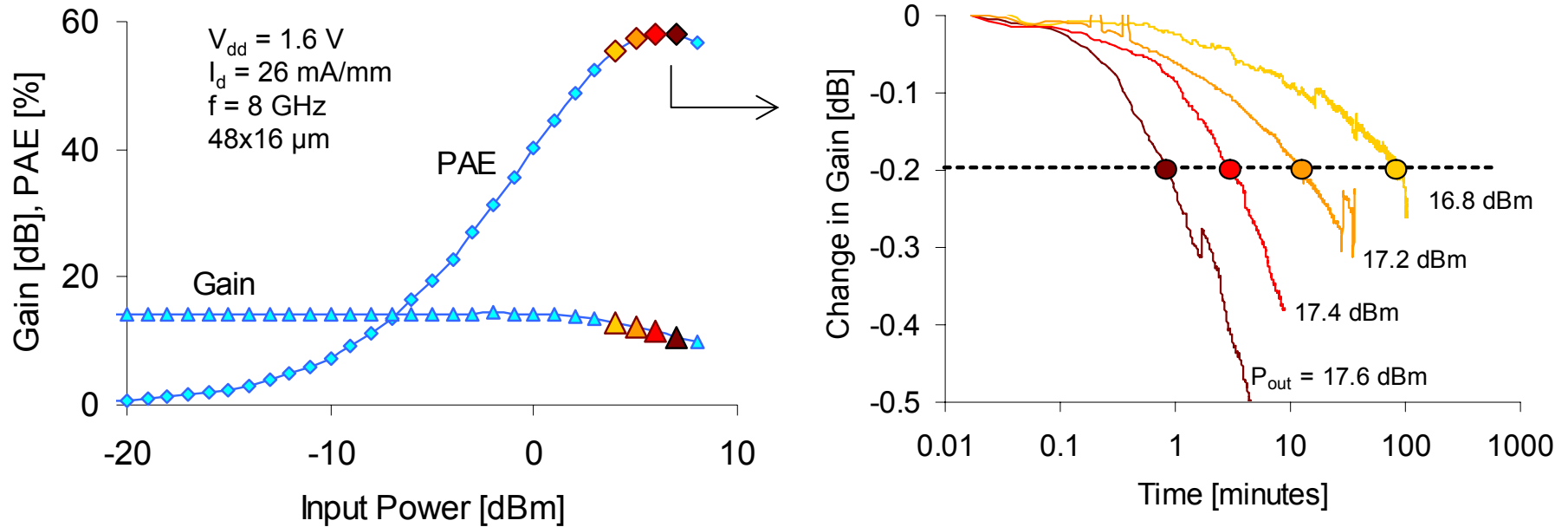


- Run device under continuous RF power conditions
- Measure drop in gain over time, define MTTF as 0.2 dB drop
- Power compression has huge impact on degradation

Reliability: impact of V_{dd}

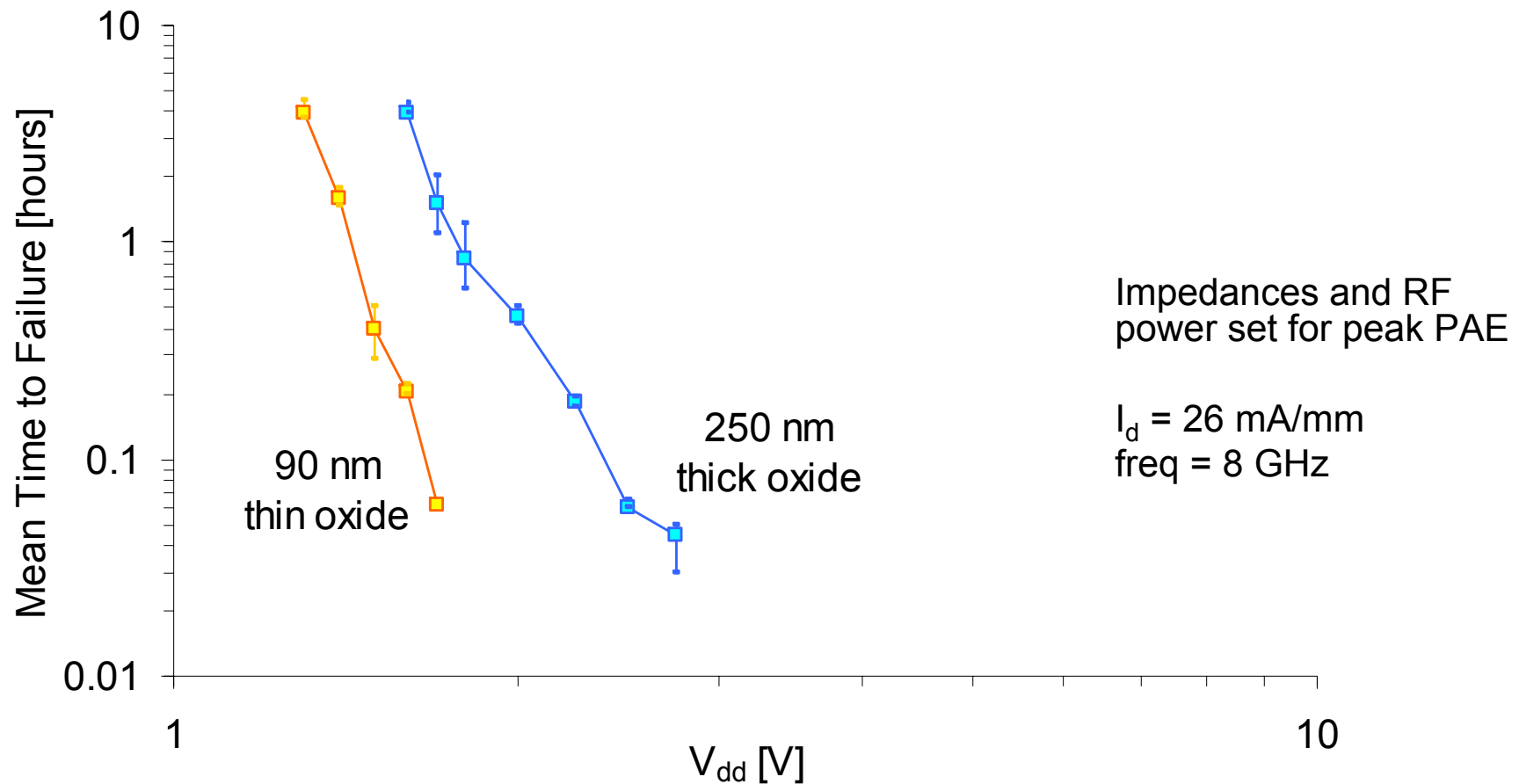

- For same V_{dd} , thick oxide is more reliable
 - but thin oxide has better performance
- For identical lifetime, how does performance compare?

Reliability: impact of V_{dd}

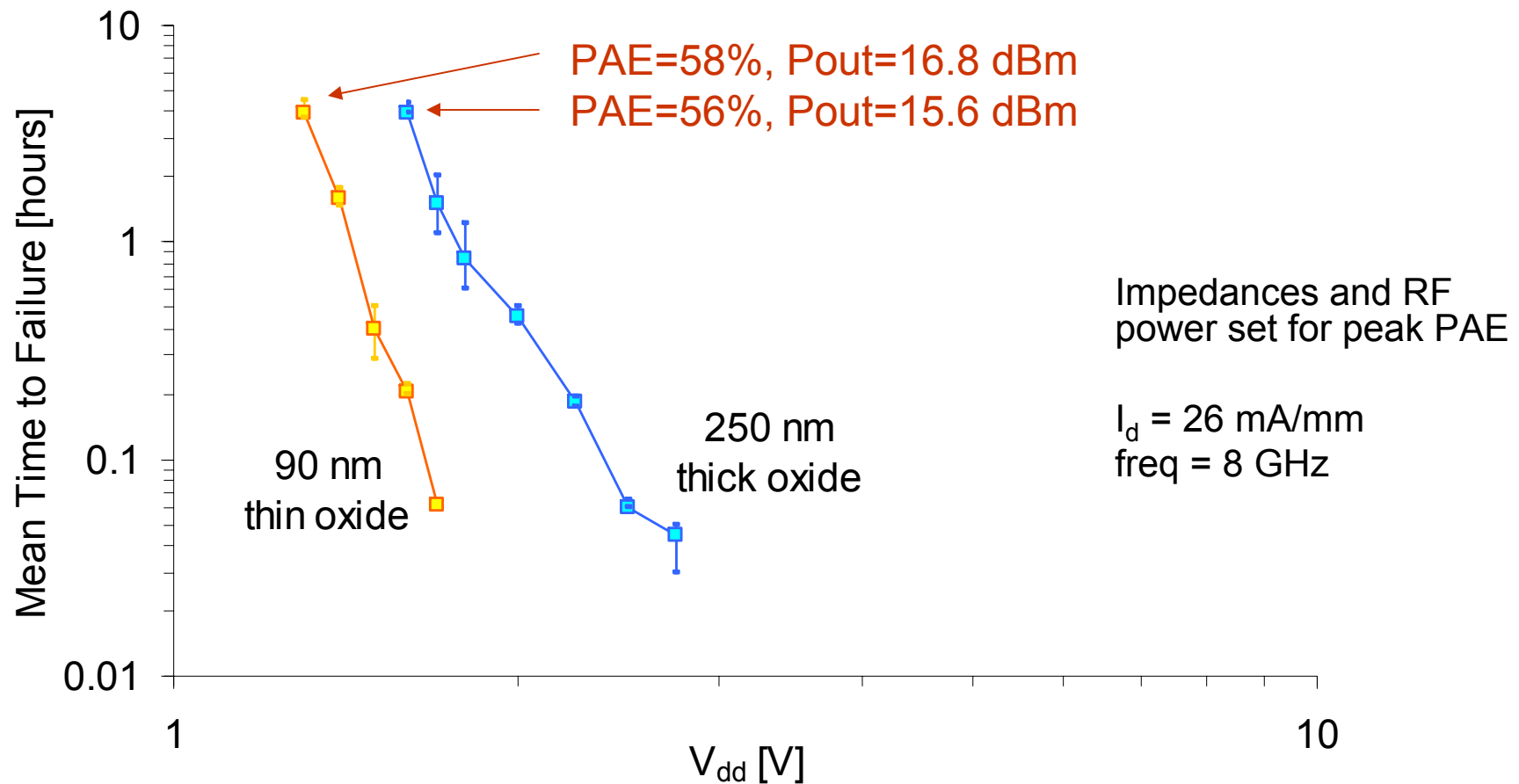


- 90 nm thin ox. outperforms 250 nm thick ox. for high MTTF
 - Low V_{dd} performance of 90 nm device much better than 250 nm device

Conclusions

- Metal-containing gates and low-loss substrates will project LDMOS to 5-6 GHz
- Deeply scaled CMOS suitable for RF power for:
 - Moderate power levels (~100 mW)
 - Very low operating voltage (~1 V and below)
- Scaling will project CMOS beyond 10 GHz
- Si-based RF power technologies will dominate many high-volume consumer applications:
 - WLANs, bluetooth, cellphone PA drivers, RF tags, etc

MIT's RF power measurement setup

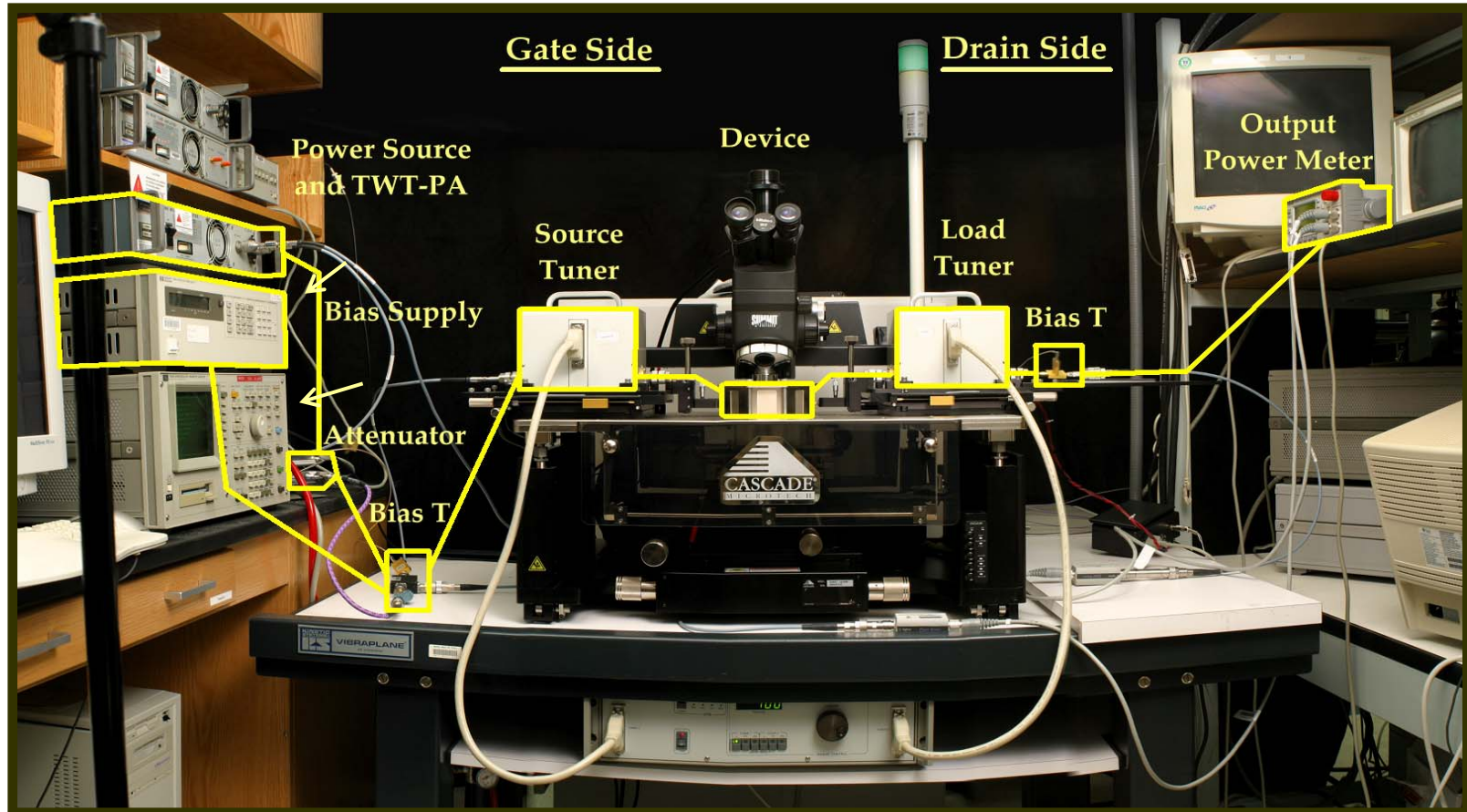

- 1.8 - 18 GHz Maury ATS automatic load-pull system
- 8-inch Cascade on-wafer probe station
- Synthesized source with 10 W TWT-PA supplying up to 200 mW at DUT

References

- LDMOS:
 - Bengtsson: MTT 2003
 - Fiorenza: SOI Conf. 1999; MTT-S 2001; IEDM 2002, EDL 2001, 2003, 2005; TED 2002
 - Scholvin: IEDM 2003
 - Van der Heijden: MTT-S 2001

- 90 nm CMOS:
 - Ferndahl: MGWL 2003
 - Scholvin: IEDM 2004